

Channel Name: Engg-Course-Made-Easy

Dear students,

Network theory (18EC32) (17EC35) (for 3rd sem ECE Branch)

Electric Circuit Analysis (18EE32) (17EE32) (for 3rd sem E&E Branch)

Network Analysis (18EI/BM/ML36) (for 3rd sem EI, Biomedical and ML Branches)

All above three are same subject with different titles. The syllabus is almost same.

**In this PDF you can find solution of previous year question papers
of**

18EC32, 17EC35 and 18EE32/17EE32




Kindly subscribe, share and Like




[Click here to SUBSCRIBE](#)




Subject: Network Theory (18EC32)




Solution for August 2021 Question paper



Click on Youtube video link to for the solution.

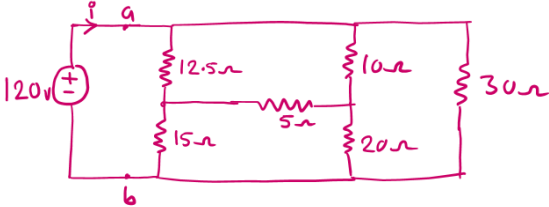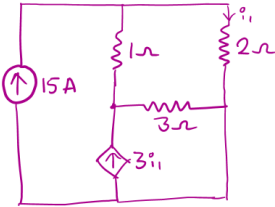
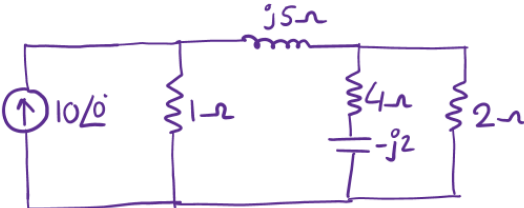
	Problem	You-Tube Link for solution
1a)	<p>Find the equivalent resistance R_{ab} for the circuit shown below and use it to find i.</p> 	https://youtu.be/fi_vzCYzIZM
1b)	<p>Determine the power supplied by the dependent source for the circuit shown below, use nodal analysis.</p> 	https://youtu.be/0i3HZPZoXVc
1c)	<p>Determine current through 2Ω resistor using mesh analysis</p> 	https://youtu.be/ZGCiuUIRiLO

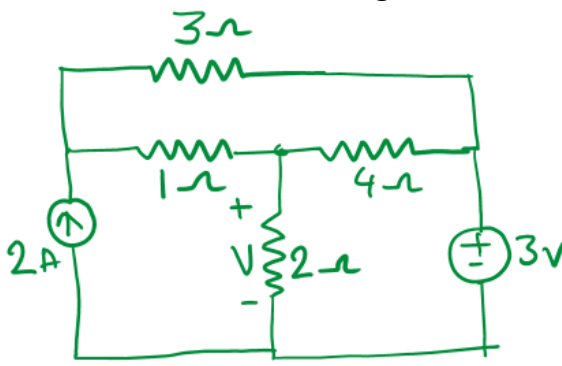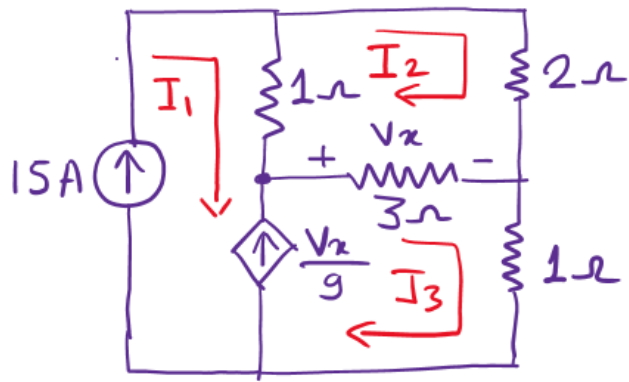
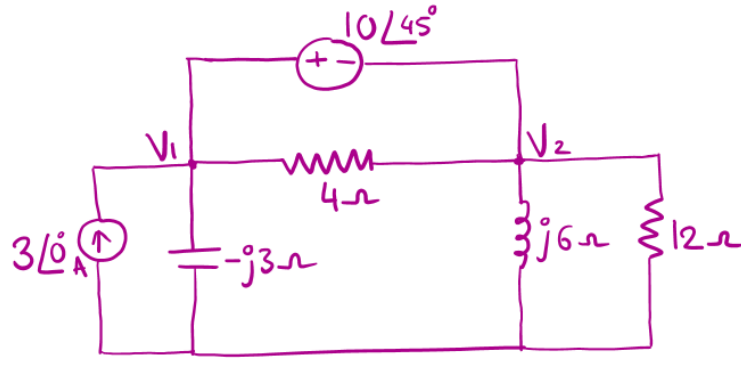
2a)	<p>Using source transformation and source shifting find current through 2Ω resistor.</p> 	<p>https://youtu.be/-IR91CwVmN4</p>
2b)	<p>Find I_1, I_2 and I_3 using mesh analysis</p> 	<p>https://youtu.be/d351w3bGfws</p>
2c)	<p>Compute V_1, V_2 in the circuit using nodal analysis.</p> 	<p>https://youtu.be/U6pWVd68qNY</p>

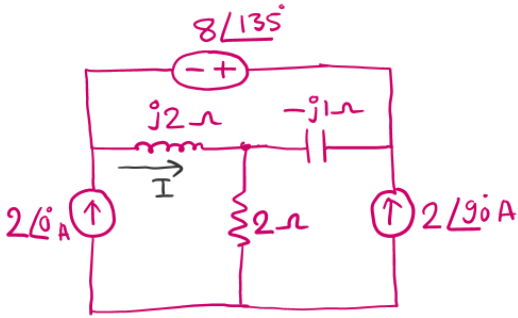
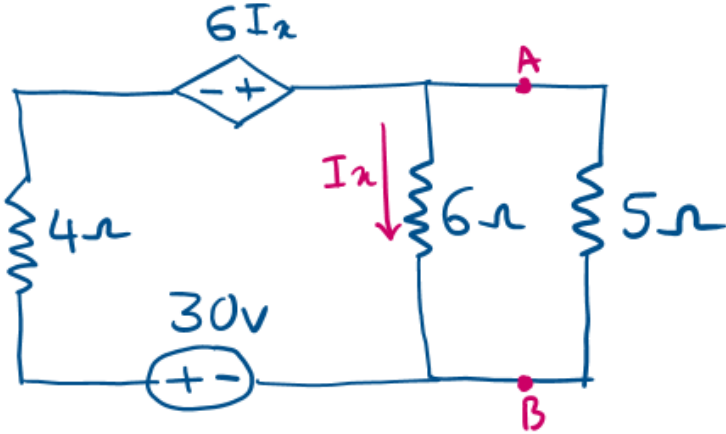
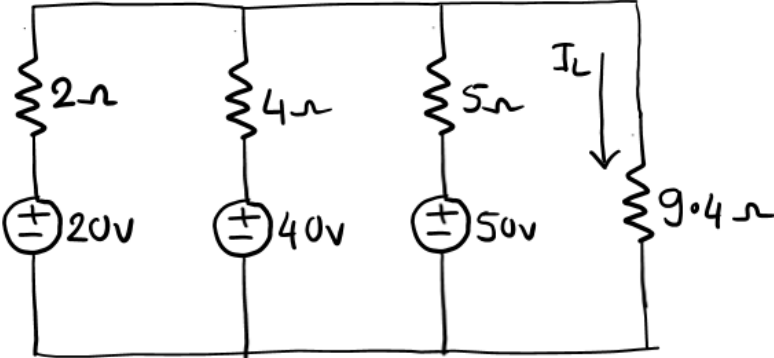
3a)	<p>For the circuit shown below, use superposition theorem to find I.</p> 	<p>https://youtu.be/VHHavIM7PjU</p>
3b)	<p>Use Norton's theorem to find current through 5Ω resistor.</p> 	<p>https://youtu.be/FY4SuLMgICs</p>
3 c)	<p>State millman's theorem. Using Millman's theorem find I_L.</p> 	<p>https://youtu.be/-w5EjIFXA_Y</p>

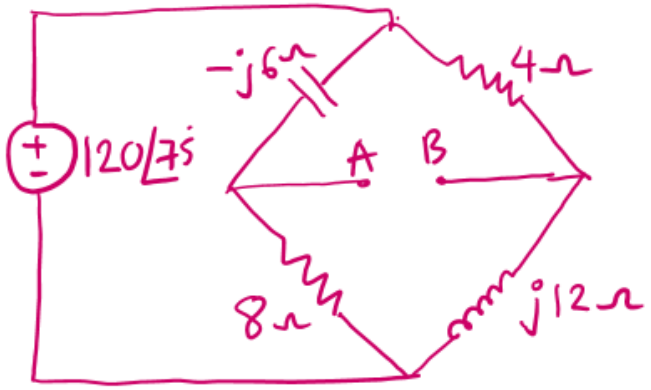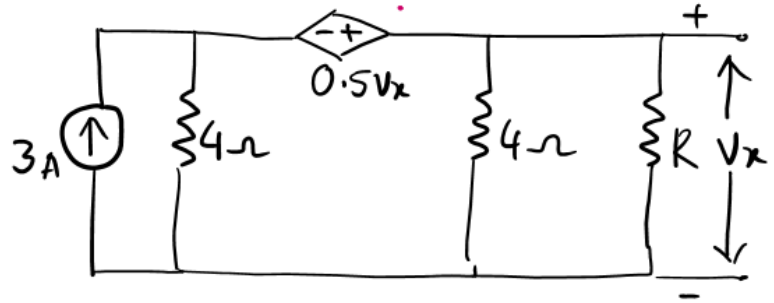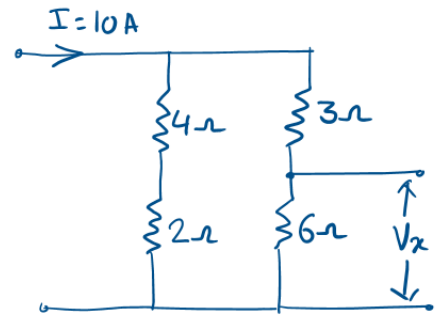4 a)	<p>Find Thevenin's equivalent at terminals AB.</p> 	<p>https://youtu.be/ObGIQ2Y_W6g</p>
4 b)	<p>Compute the value of R that results in maximum power to it in figure shown below. Find the maximum power.</p> 	<p>https://youtu.be/HSX1Cbi8dJg</p>
4 c)	<p>State Reciprocity theorem. Find V_x and verify reciprocity theorem for the circuit shown below.</p> 	<p>https://youtu.be/QzD6GLs1yQw (reciprocity thm)</p> <p>https://youtu.be/-w5EjIFXA_Y</p>

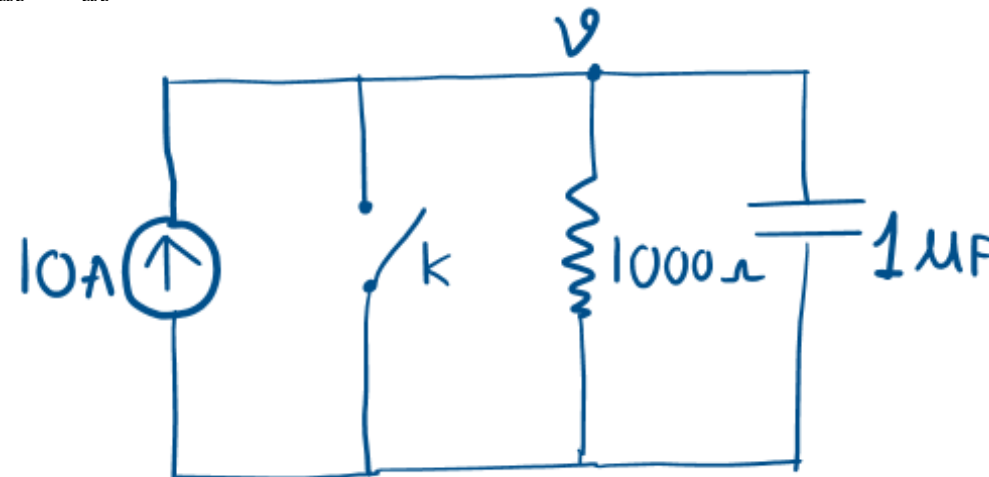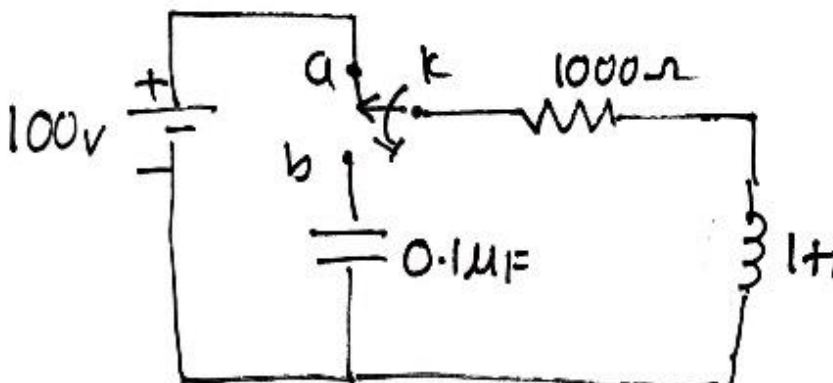5 a)	<p>In the network shown below, the switch k is opened at $t = 0$. At $t = 0^+$ solve for v, $\frac{dv}{dt}$, $\frac{d^2v}{dt^2}$.</p> 	<p>https://youtu.be/YG6yX1KOKfc</p>
5 b)	<p>In the network shown below, the switch is changed position from 1 to 2 at $t = 0$, the steady state is reached before switching. Calculate i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.</p>	<p>https://youtu.be/2jDIYHIU0VM</p>
6 a)	<p>In the network shown below, the switch k is changed position from a to b at $t = 0$. Solve for i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. The steady state having reached before switching.</p> 	<p>https://youtu.be/GQWYGQ_gqg0</p>

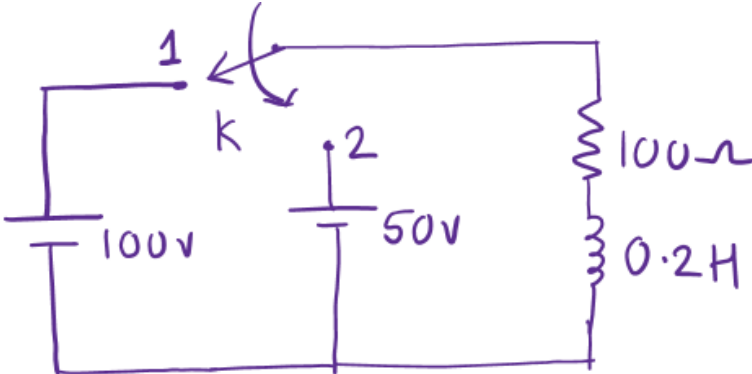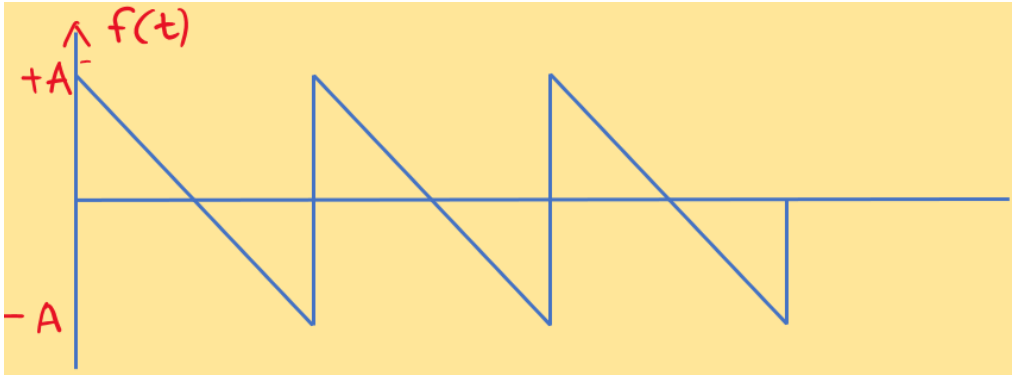6 b)	<p>In the network shown below, the switch k is closed at $t=0$, with zero capacitor voltage and zero inductor current. Solve for a) V_1 and V_2 at $t=0^+$, b) V_1 and V_2 at $t=\infty$ c) $\frac{dv_1}{dt}, \frac{dv_2}{dt}$ at $t=0^+$ $\frac{d^2v_2}{dt^2}$ at $t=0^+$</p>	https://youtu.be/m11iom05SXc
7 a)	<p>In the circuit shown below, switch is closed on position 1 at $t=0$ and $t=500\mu s$, switch is moved to position 2. Obtain equation of current in both intervals. Use Laplace transforms.</p> 	https://youtu.be/KX9Q4m869go
7 b)	<p>Determine the Laplace transform of periodic saw tooth waveform as shown in fig. below</p> 	https://youtu.be/VlzpPoT-gms

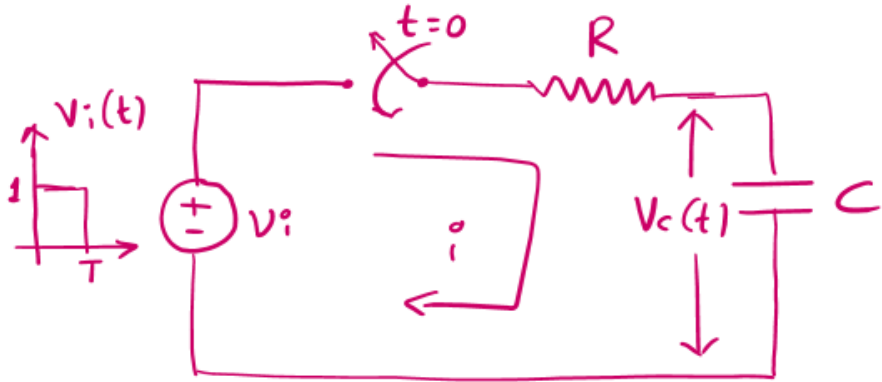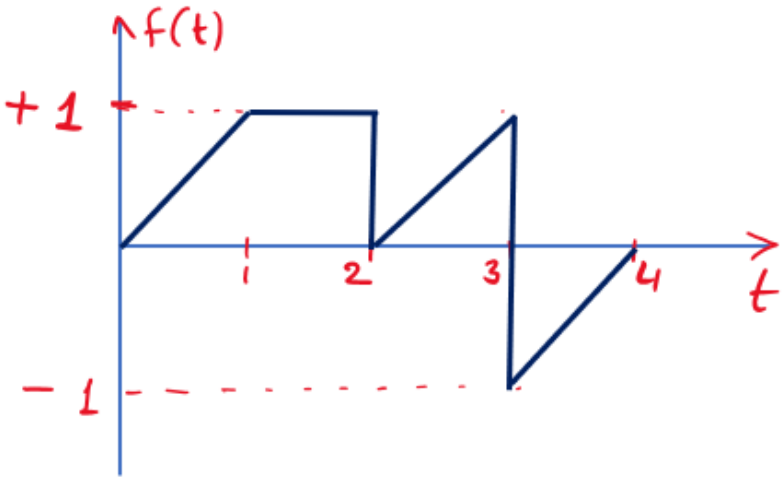8 a)	<p>A voltage of unit height and width T is applied to the circuit shown below at $t=0$. Determine Voltage across capacitance C as a function of time.</p> 	https://youtu.be/PgNK_MrEbPQ
8 b)	<p>Determine the Laplace transform of the waveform shown below.</p> 	https://youtu.be/yLmveB0zRPs
9 a)	<p>With respect to series resonant circuit show that resonant frequency is the geometric mean of two half power frequencies</p>	https://youtu.be/E6Gd9JDngnw
9 b)	<p>A series resonant circuit includes $1\mu\text{F}$ capacitor, resistance of 16Ω and an inductance of L henry. If the bandwidth is 500rad/sec, determine i) ω_r ii) Q iii) L</p>	https://youtu.be/S411KAr7b3w

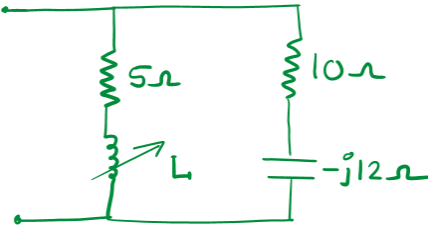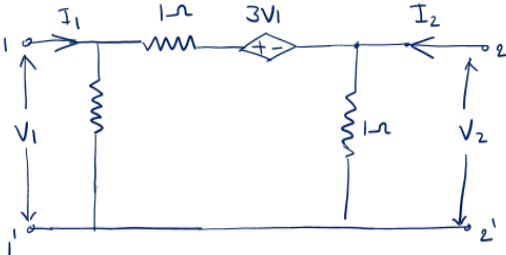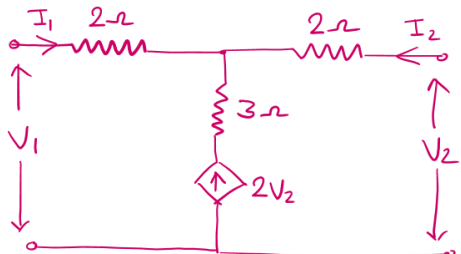9 c)	<p>Find the value of L for which the circuit resonates at frequency of 1000rad/sec for the circuit shown below.</p> 	https://youtu.be/73NhM9p_03o
10 a)	Derive Z parameters in terms of H parameters.	https://youtu.be/pZ4O_mxW8EM
10 b)	<p>Determine Z parameters of the network shown below.</p> 	https://youtu.be/D4YXr5QiQgw
10c)	<p>For the network shown below, find Y parameters.</p> 	https://youtu.be/-TpT-LVpeSI



Kindly subscribe to see more videos on this subject.




[Click here to SUBSCRIBE](#)




Subject: Network Theory (18EC32)




Solution for Jan./Feb.2021 Question paper




Click on Youtube video link to for the solution.


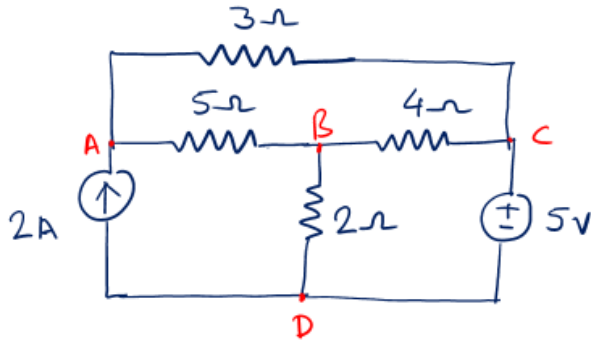
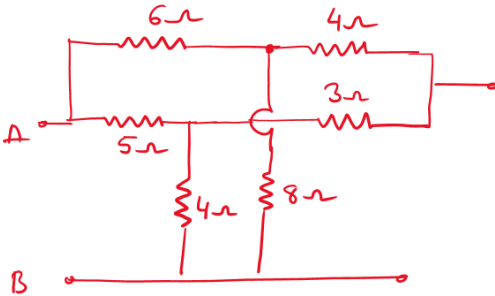
	Problem	You-Tube Link for solution
1 a)	<p>Using Source transformation and source shifting techniques find voltage across 2Ω resistor for the given circuit.</p> 	<p>https://youtu.be/9L47CrS6aq0</p>
1 b)	<p>Find equivalent resistance between A and B using star delta transformation</p> 	<p>https://youtu.be/UoMMMy60juls</p>

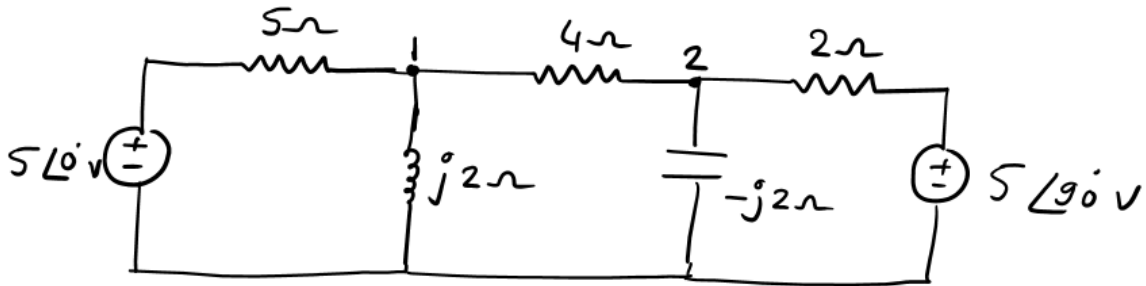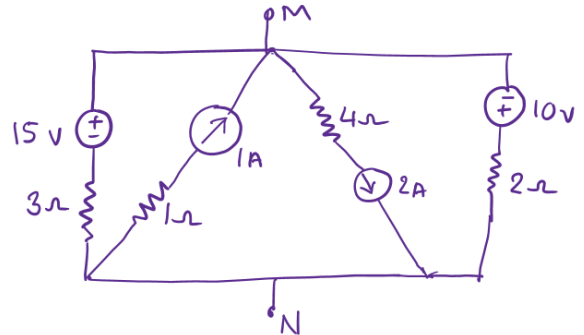
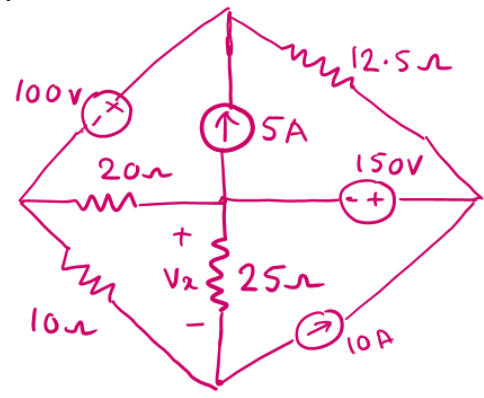
1 c)	<p>Determine the Node voltages V_1 and V_2 by nodal analysis for the network shown below.</p> 	<p>https://youtu.be/diuuoUBBU4k</p>
2 a)	<p>Find the potential difference between M and N using source transformation for the circuit shown below.</p> 	<p>https://youtu.be/SRgdUKmOL04</p>
2 b)	<p>Find V_x using nodal analysis</p> 	<p>https://youtu.be/Hj3CZNqyW1g</p>

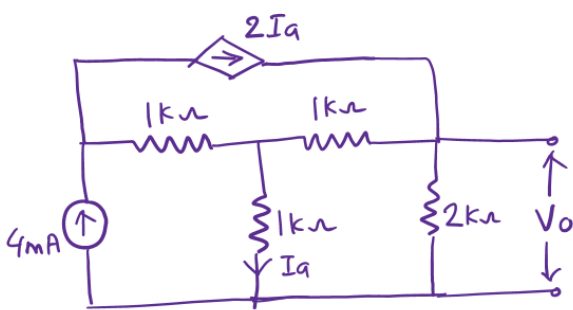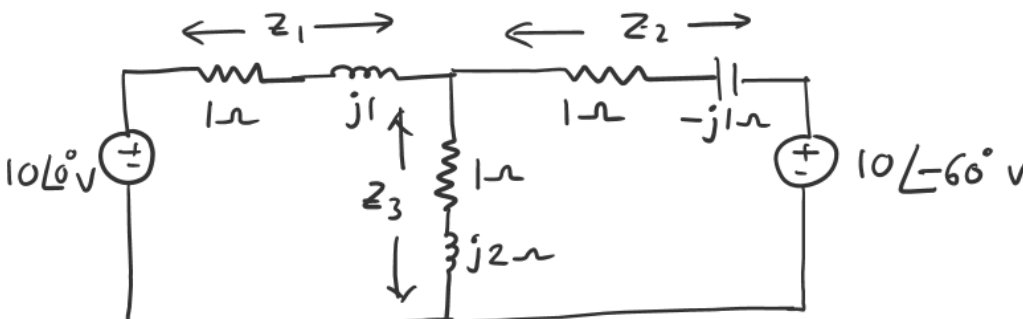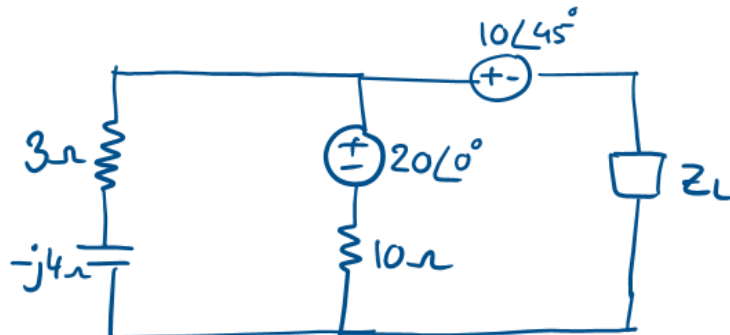
2 c)	<p>Determine V_o using mesh analysis for the network shown below.</p> 	<p>https://youtu.be/x9p6VRIsPOs</p>
3 a)	<p>State and prove millman's theorem.</p>	<p>https://youtu.be/a5HT5WRCMY</p>
3 b)	<p>Find current through Z_3 using superposition theorem</p> 	<p>https://youtu.be/EV3DcATjzE0</p>
3 c)	<p>Find the value of Z_L for which maximum power transfer occurs in the network shown below.</p> 	<p>https://youtu.be/aiBstMqbPC8</p>

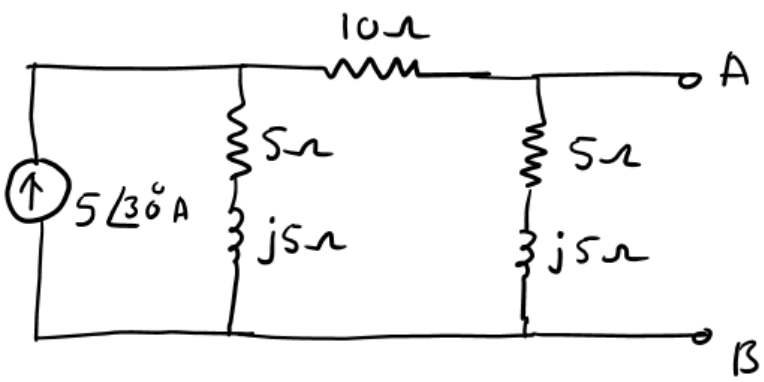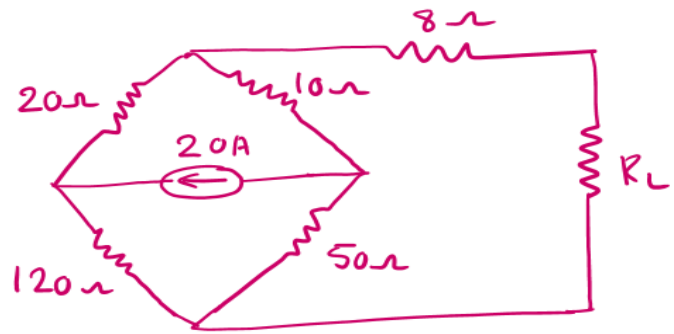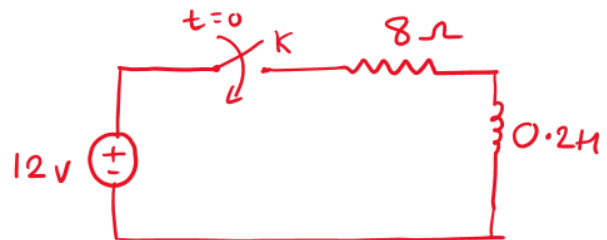4 a)	<p>Find Thevenin's and Norton's equivalent for the circuit Shown below hence find current through $10\ \Omega$ resistor across AB.</p> 	<p>https://youtu.be/AJmT4OIziyl</p>
4 b)	<p>Find the value of R_L for which maximum power is delivered. Also find the maximum power that is delivered to the load.</p> 	<p>https://youtu.be/Mztn6NNp2eo</p>
5 a)	<p>In the network shown below switch k is closed at $t=0$ with zero current in the inductor.</p> <p>Find i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$</p> 	<p>https://youtu.be/hMpWw0SUQW0</p>

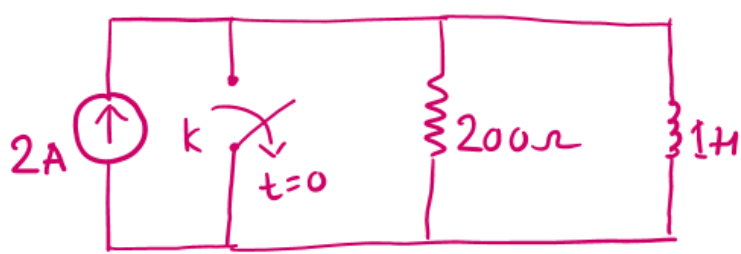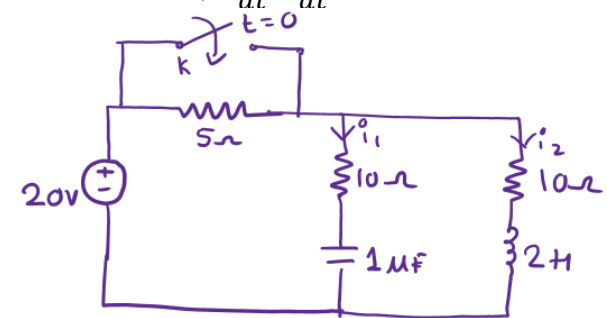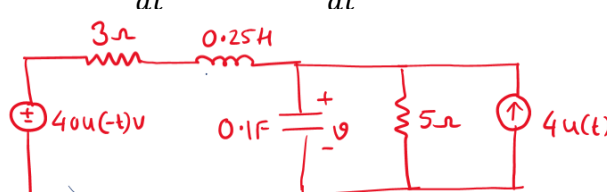5 b)	<p>In the network shown below, the switch is changed position from 1 to 2 at $t = 0$, the steady state is reached before switching. Calculate i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.</p>	<p>https://youtu.be/s_dSHq1xdPE</p>
5 c)	<p>In the network shown below, the switch k is opened at $t = 0$. At $t = 0^+$ solve for v, $\frac{dv}{dt}$, $\frac{d^2v}{dt^2}$</p> 	<p>https://youtu.be/aqgFJA4bVfU</p>
6 a)	<p>For the circuit shown below, steady state is reached with switch k open. The switch is closed at $t=0$. Find $i_1, i_2, \frac{di_1}{dt}, \frac{di_2}{dt}$ at $t = 0^+$</p> 	<p>https://youtu.be/2q2HLhDn_9E</p>
6 b)	<p>For the circuit shown below, i) $v(0^+)$ and $i(0^+)$ ii) $\frac{dv(0^+)}{dt}$, and $\frac{di(0^+)}{dt}$ iii) $v(\infty)$ and $i(\infty)$</p> 	<p>https://youtu.be/IMB8nqilpdk</p>

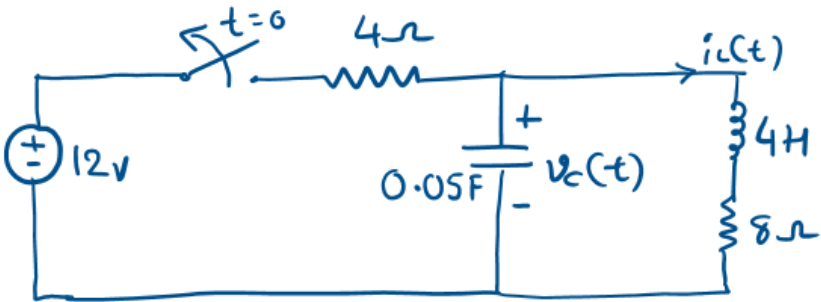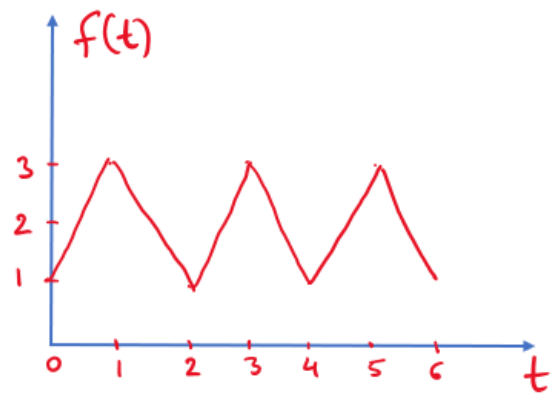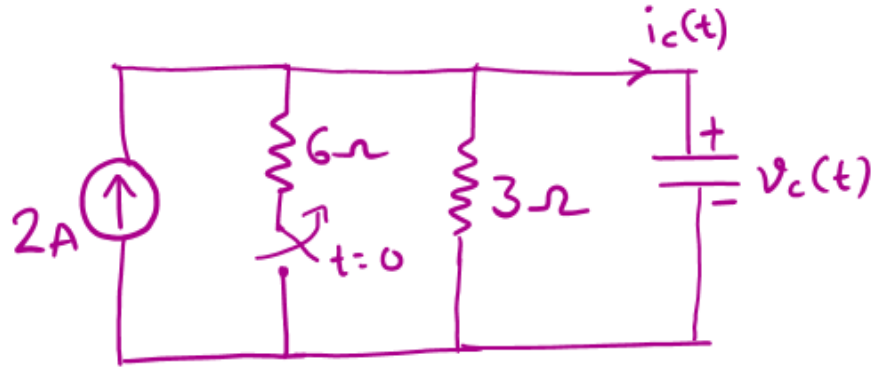7 a)	<p>Determine current $i(t)$ for $t \geq 0$ for the circuit shown below.</p> 	<p>https://youtu.be/RwLyhIkZgbw</p>
7 b)	<p>Find the Laplace transform of the function $f(t)$ shown below.</p> 	<p>https://youtu.be/x4UFLg8Tif8</p>
8 a)	<p>Determine $v_C(t)$ and the current $i_C(t)$ for $t \geq 0$ for the circuit shown below.</p> 	<p>https://youtu.be/sqyQ6dC_4Fw</p>

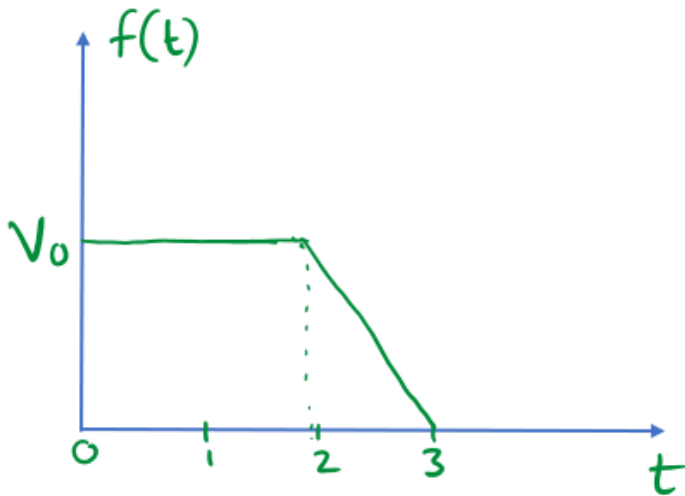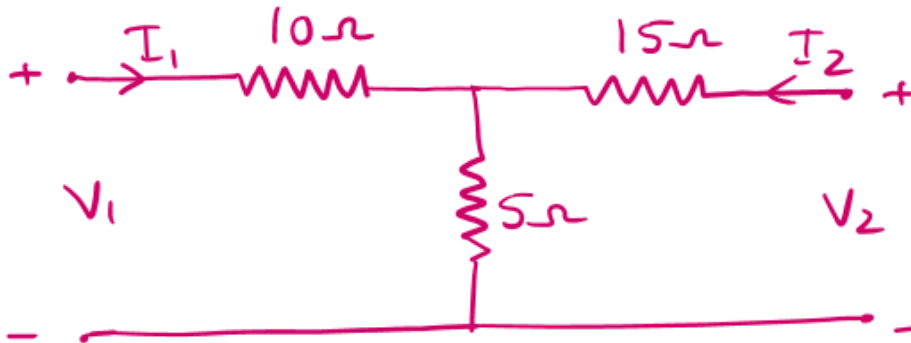8 b)	<p>Find Laplace transform of $f(t)$ shown below.</p> 	https://youtu.be/qlQAt3_BG0I
9 a)	Express Y parameters in terms of H parameters	https://youtu.be/DiEXO4-o-Q
9 b)	<p>Find Z parameters for the network shown below.</p> 	https://youtu.be/ayKFyQnB7XE
9 c)	The Z parameters of two port network are $Z_{11} = 20\Omega$, $Z_{22} = 30\Omega$, $Z_{12} = Z_{21} = 10\Omega$. Find Y and ABCD parameters.	https://youtu.be/Yf-blZ8dbT8
10 a)	Prove that resonant frequency is the geometric mean of two half power frequencies.	https://youtu.be/E6Gd9JDngnw

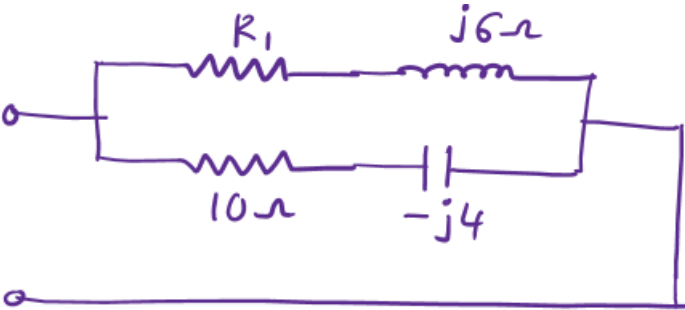10 b)	<p>A series RLC circuit has a resistance of 10Ω, $L= 0.01\text{H}$ and $C=0.01\mu\text{F}$ and is connected across 10mv supply. Calculate i) f_0 ii) Q_0 iii) Bandwidth iv) f_1 and f_2 v) I_0</p>	<p>https://youtu.be/7alcR23Uh3c</p>
10c)	<p>Find the value of R_L such that the circuit shown below is resonant.</p> 	<p>https://youtu.be/sqp1rzi-0HU</p>

Kindly subscribe to see more videos on this subject.



[Click here to SUBSCRIBE](#)




Channel Name: Engg-Course-Made-Easy [SUBSCRIBE](#)



Subject: Network Theory (18EC32)



Solution for Dec.2019/Jan.2020 Question paper




Click on Youtube video link to for the solution.


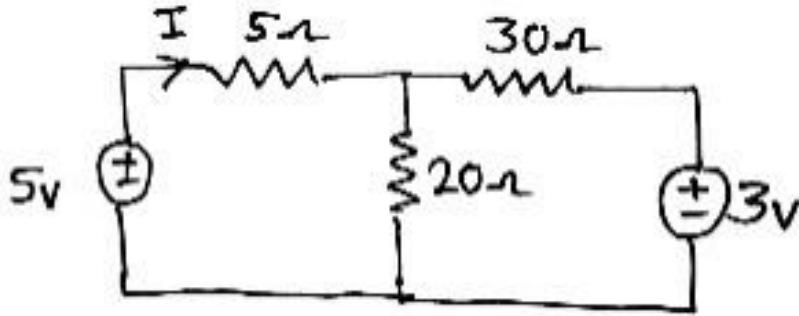
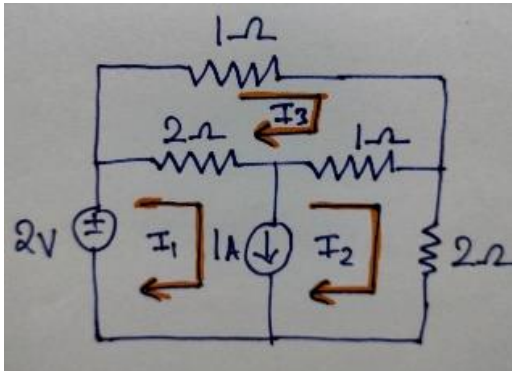
1 a)	<p>Using Source transformation technique find the current through 5Ω resistor for the given circuit.</p> 	<p><u>https://youtu.be/lKXEtbcMsdA</u></p>
1 b)	<p>Use Mesh Analysis to Determine current i_1, i_2, i_3</p> 	<p><u>https://youtu.be/bDsgn6DDJ9I</u></p>

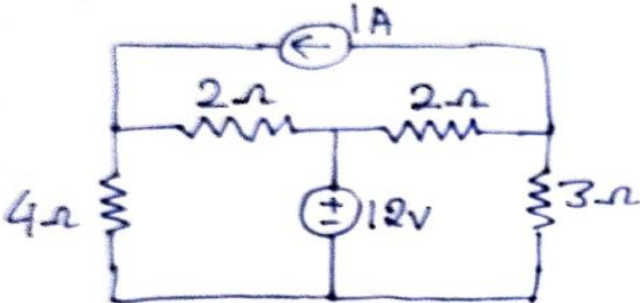
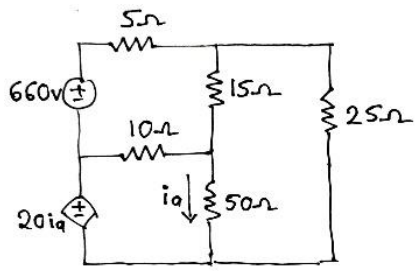
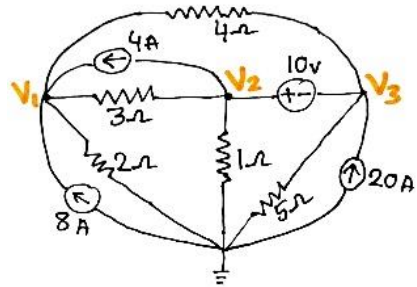
1 c)	<p>Find the power delivered by 1A current source using Nodal analysis for the circuit shown below</p> 	<p>https://youtu.be/vMqq8H1tIUc</p>
2 a)	<p>Three impedances are connected in delta, obtain the star equivalent of the network.</p>	<p>https://youtu.be/e-dh529iJAU</p>
2 b)	<p>Use Mesh Analysis to Find power delivered by the dependent voltage source in the circuit shown below</p> 	<p>https://youtu.be/VKvfgwNiDQw</p>
2 c)	<p>Determine all the Node voltages for the circuit shown below, using nodal analysis.</p> 	<p>https://youtu.be/y46CjpRU4s4</p>

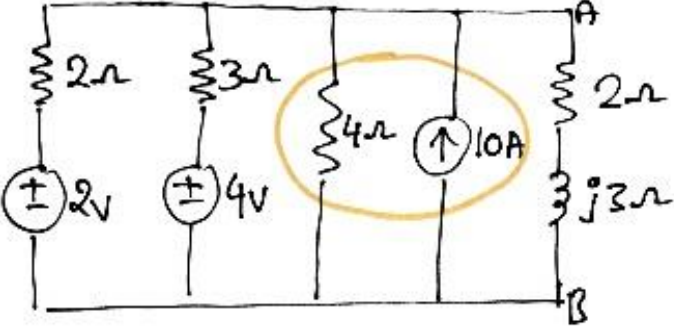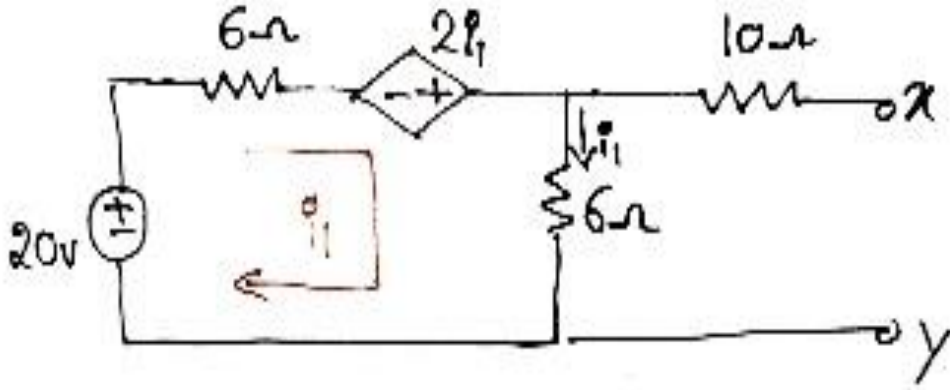3 a)	State and explain superposition theorem.	https://youtu.be/QEH8LObMICE
3 b)	<p>Use Millman's theorem to find the current flowing through $(2+j3)\Omega$ impedance for the circuit shown below.</p> 	https://youtu.be/QTEpFBHl6eU
3 c)	State and prove Norton's theorem	https://youtu.be/Y3HbrL04RXM
4 a)	<p>Find Thevenin's equivalent for the circuit Shown below with respect to terminals X-Y</p> 	https://youtu.be/MQCjhE0Lsp0
4b)	Find condition for maximum power transfer in AC circuit, where both RL and XL are varying.	https://youtu.be/i8269fBfNXY

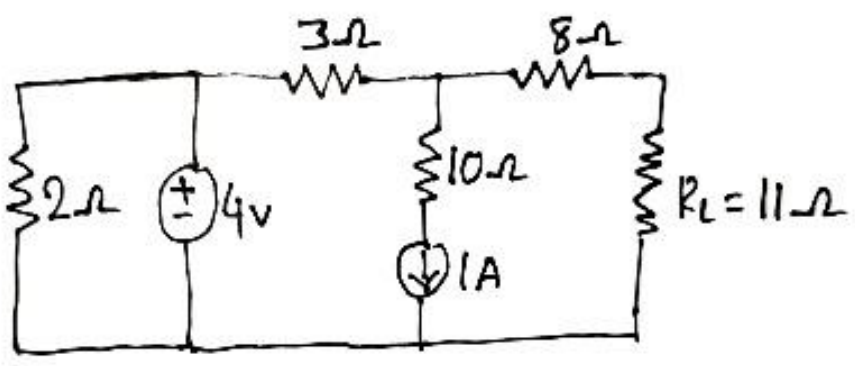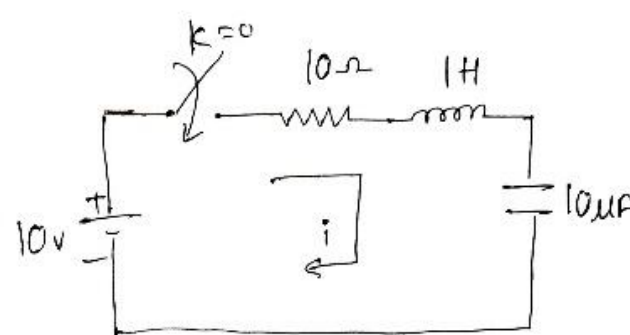4 c)	<p>Determine the current through the load resistance using Norton's theorem</p> 	<p>https://youtu.be/_1IfyGAKfqQ</p>
5a)	<p>Explain the behavior of RLC elements at the time of switching at $t=0$, at $t=0+$ at $t=\infty$</p>	
5 b)	<p>Find i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume that capacitor is initially uncharged.</p> 	<p>https://youtu.be/EgSvdYZ9-LY</p>

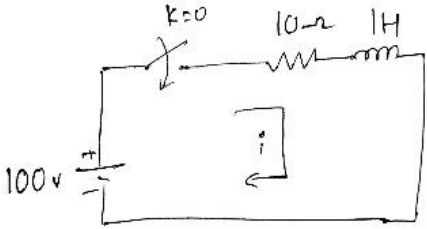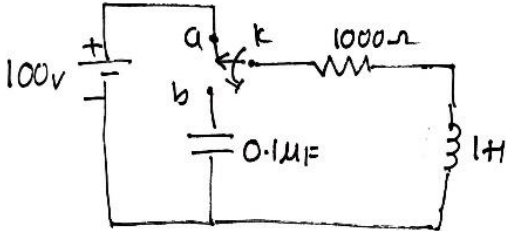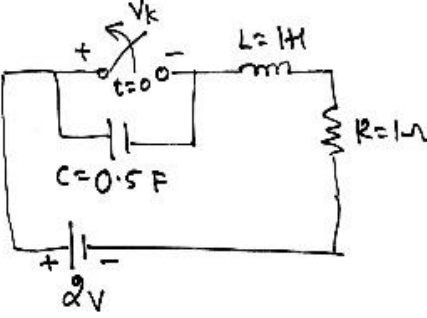5 c)	<p>Find i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. The switch is closed at $t = 0$ with zero current in the inductor.</p> 	<p>https://youtu.be/UtTK_Vc2eV8</p>
6 a)	<p>In the network shown below, the switch k is changed position from a to b at $t = 0$, the steady state is reached at position a. Find i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume that the capacitor is initially uncharged.</p> 	<p>https://youtu.be/GQWYGQ_gqg0</p>
6 b)	<p>For the network shown below, the network is steady state with switch k closed. At $t = 0$, switch is opened. Determine voltage across switch V_k, $\frac{dV_k}{dt}$, at $t = 0^+$.</p> 	<p>https://youtu.be/vnHiwGEJSVA</p>

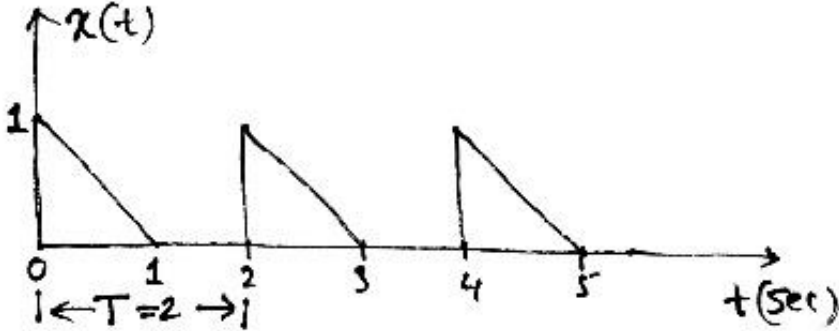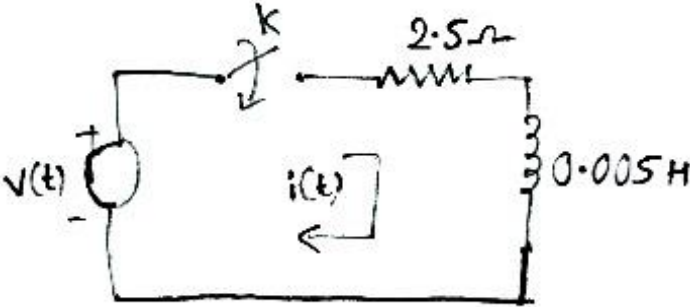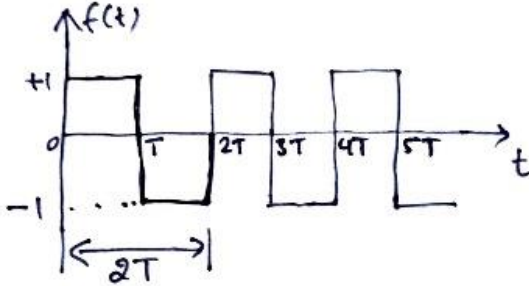7 b)	<p>Find Laplace Transform of the periodic signal $x(t)$, shown below.</p> 	<p>https://youtu.be/hxG44NC0HTY</p>
8 a)	<p>In the series RL circuit shown, the source voltage is $V(t)=50\sin 250t$ V. Using Laplace Transform the current when switch k is closed at $t=0$.</p> 	<p>https://youtu.be/nAmrV_drQz8</p>
8 b)	<p>Find Laplace Transform of the non-sinusoidal periodic waveform.</p> 	<p>https://youtu.be/OcjdYov6204</p>

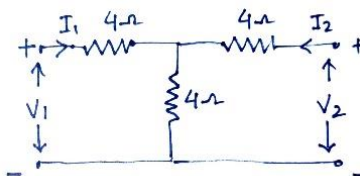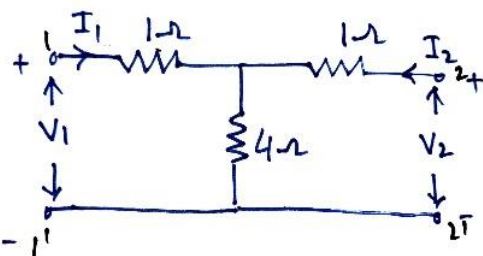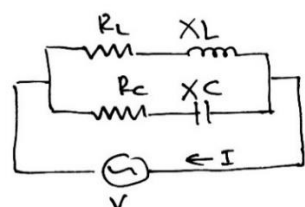9a)	Define Z parameters. Determine Z parameters in terms of Y parameters	https://youtu.be/ro55flsznd8
9 b)	Determine h Parameters of the given circuit. 	https://youtu.be/253teZ4LvDw
9 c)	Find Transmission (T) Parameters 	https://youtu.be/5FDmyR1x8IU
10a)	Define Q factor, Selectivity and Bandwidth	
10b)	A series RLC circuit has a resistance of 10Ω , an inductance of $0.3H$ and a capacitance of $100\mu F$. The applied voltage is $230V$. Find Resonance frequency, Lower & upper cutoff frequencies current at resonance, current at f_1 & f_2 , Voltage across inductance at resonance.	https://youtu.be/qCivWKXpuRQ
10c)	Derive the expression for the resonant frequency of the circuit shown below. Also show that the circuit will resonate at all frequencies if $RL = RC = \sqrt{\frac{L}{C}}$ 	https://youtu.be/mY9Zvi2x2mk

Kindly subscribe to see more videos on this subject.



[Click here to SUBSCRIBE](#)

Channel Name: **Engg-Course-Made-Easy** [SUBSCRIBE](#)


Subject: Network Theory (Network Analysis) (17EC35)

Solution for Dec.2018/Jan.2019 Question paper

Click on corresponding You-tube video link to for the solution.

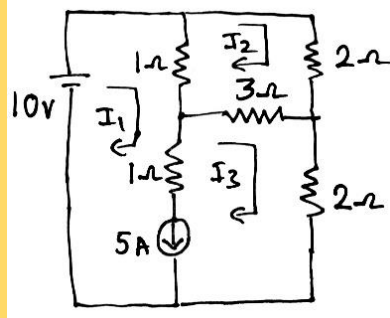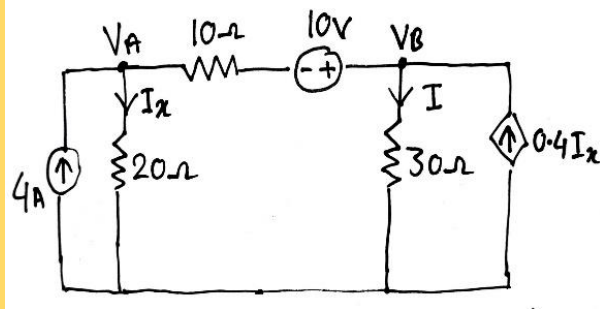
	Problem	You-Tube Link for solution
1 a)	Reduce the Network shown below to a single voltage source in series with a resistance using source shift and source transformation.	<u>https://youtu.be/oCVh8GcEKGg</u>
1 b)	Use mesh analysis to determine the three mesh currents 	<u>https://youtu.be/zyFZbYw8_dM</u>
1 c)	Find current in 30 Ω resistor using nodal analysis for the circuit shown below 	<u>https://youtu.be/jlkWyCkjNks</u>

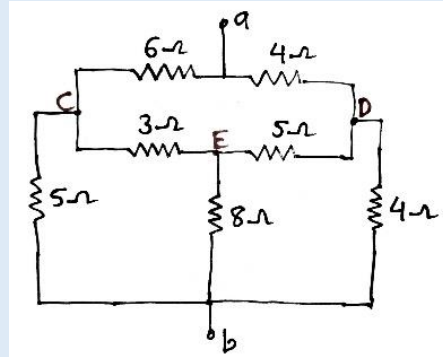Find the equivalent resistance between a and b using star delta transformation




<https://youtu.be/vOLM2ekc28w>

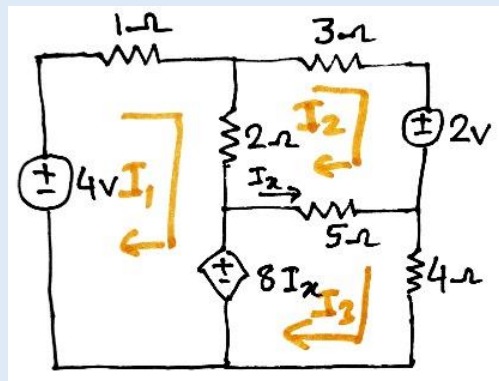For the circuit shown below, determine I_x , and other loop currents



<https://youtu.be/eL5Njc6pS14>

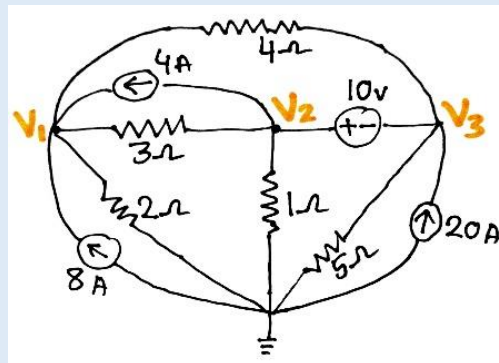
For the circuit shown below, determine all node voltages.



<https://youtu.be/y46CjpRU4s4>

3 a)

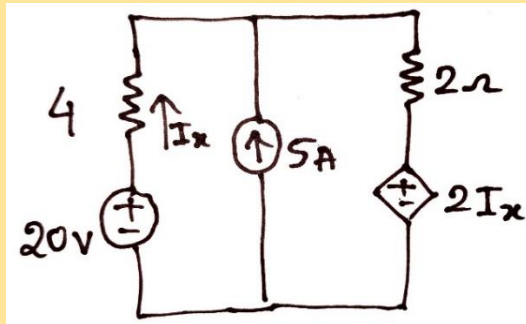
For the circuit shown in below, find the current I_x , using super position theorem



https://youtu.be/IcASlZ_cnDQ

3 c)

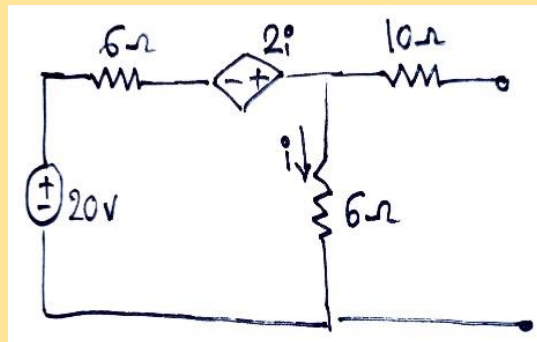
Obtain the Thevenin's equivalent of the circuit shown below





<https://youtu.be/WJZhyf0439Q>

4 a)

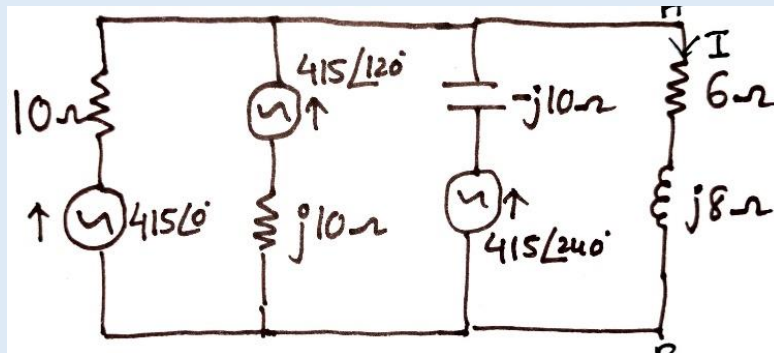For the circuit shown below, find the current in $(6 + j8)\ \Omega$ impedance using Millman's theorem.




<https://youtu.be/G-cP-BGLyhM>

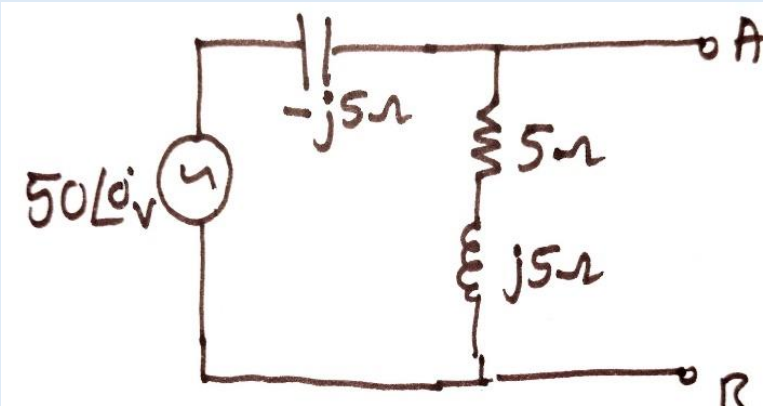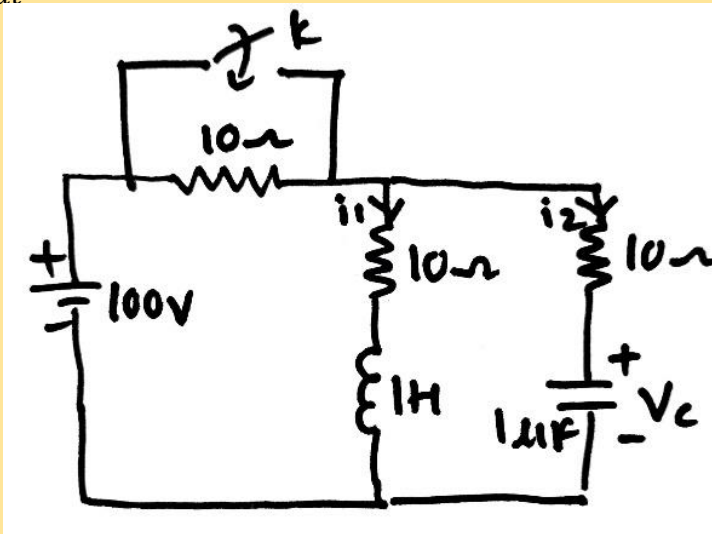4 b)	<p>For the Network shown below, determine Norton's equivalent across A and B. Find the current through the impedance $(6 - j8) \Omega$ connected to the terminals A and B</p> 	<p>https://youtu.be/Vg0iwVmqZkM</p>
4 c)	<p>State and prove maximum power transfer theorem for AC circuit, where both RL and XL are varying.</p>	<p>https://youtu.be/i8269fBfNXY</p>
5 a)	<p>In the network shown below, a steady state is reached with the switch K open. At $t = 0$, the switch K is closed. Obtain the initial values of Find i_1, i_2, V_c, $\frac{di_1}{dt}$, $\frac{di_2}{dt}$ and $\frac{dV_c}{dt}$ at $t = \infty$</p> 	<p>https://youtu.be/2jDIYHIU0VM</p>

5 b)

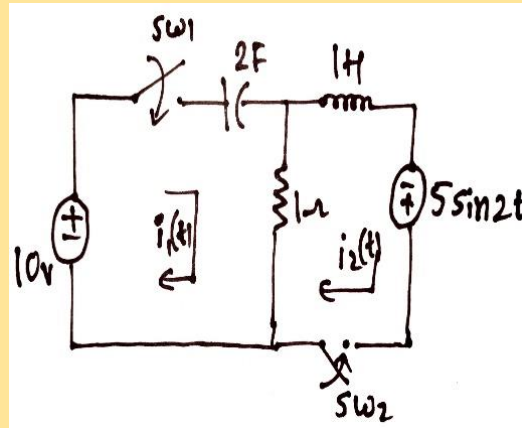
For the given circuit, find the value of the loop currents, their first derivatives and their 2nd derivatives, all evaluated at $t = 0+$, given that $V_c(0-) = 1$ volts, $i_2(0-) = 0$ amp. At $t = 0$, sw1, and sw2 are closed.



<https://youtu.be/2swnQfKZu0Y>

6 a)

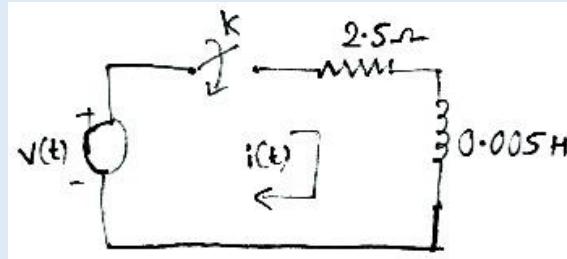
In the circuit shown below, the source voltage is $V(t) = 50\sin 250t$ V. Using Laplace Transform determine current when switch k is closed at $t = 0$.



https://youtu.be/nAmrV_drQz8

6 b)

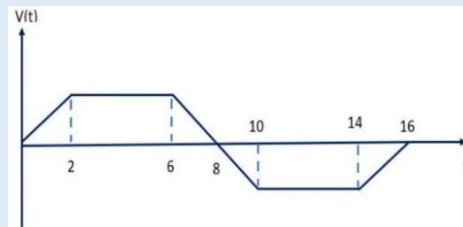
Synthesize the periodic waveform shown below, find its Laplace transform and prove any formula used.





<https://youtu.be/mCWLY5VmvkU>

Proof for the formula used

<https://youtu.be/0aAZlZLThxc>

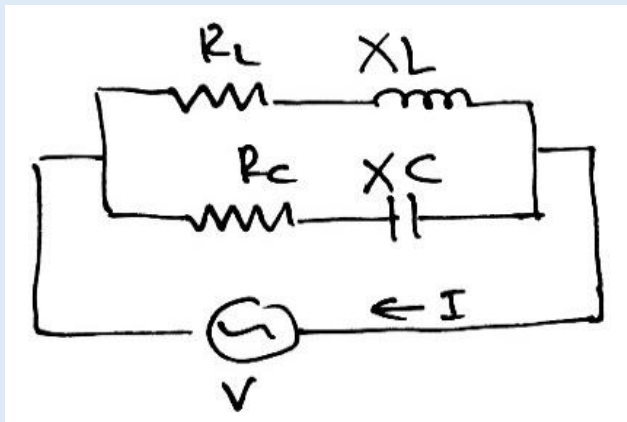7 a)	Show that resonant frequency of series resonant circuit is equal to the geometric mean of two half power frequencies.	https://youtu.be/E6Gd9JDngnw
7 b)	A coil is connected in series with a variable capacitor across $V(t) = 10 \cos 1000t$. The current is maximum when $c = 10\mu\text{F}$. When $C = 12.5\mu\text{F}$, the current is 0.707 times the maximum value. Find L , R and Q of the coil.	https://youtu.be/Rq9kLS9zMTU
7 c)	A coil has resistance of 400Ω and inductance of $318\mu\text{H}$. Find the capacitance of capacitor which when connected in parallel with the coil will produce resonance with a supply frequency of 1MHz . If a second capacitor of capacitance 23.42pF is connected in parallel with the first capacitor, find the frequency at which resonance will occur.	https://youtu.be/szWi9UrEjgI
8 a)	<p>Derive the expression for the resonant frequency of the circuit shown below. Also show that the circuit will resonate at all frequencies if $RL = Rc = \sqrt{\frac{L}{C}}$</p> 	https://youtu.be/mY9Zvi2x2mk
8 b)	A coil of 10Ω resistance 0.2H inductance is connected in parallel with a variable condenser across 220V , 50Hz supply. Determine: (i) Capacitance of condenser so that current drawn may be in phase with the supply voltage (ii) Effective impedance of the circuit (iii) Power absorbed at resonance (iv) Current magnification factor.	https://youtu.be/n47bR1zSlRk

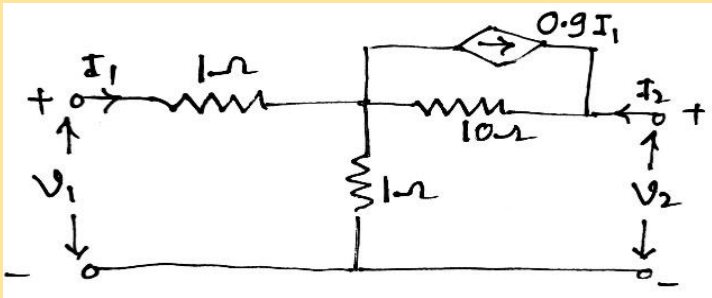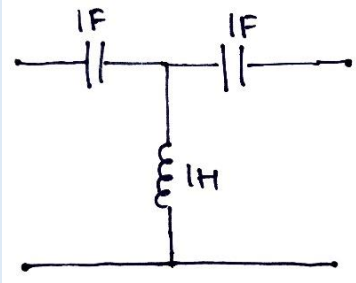9 a)	<p>Z-parameters of a network are obtained from an experiment. Explain how Y-parameters parameters can be computed from the experiment data.</p>	https://youtu.be/LTxQBrd4EHo
	<p>Explain how T-parameters parameters can be computed from the experiment data.</p>	https://youtu.be/R9cSwgKcvhM
9 b)	<p>Find Z & Y parameters of the network shown below.</p> 	https://youtu.be/3BkWYHHqkgc
10a)	<p>Find Z and H parameters for the network shown below.</p> 	https://youtu.be/djdUj_s8yG4
10c)	<p>Explain symmetry and reciprocal property of 2 port network</p>	https://youtu.be/UhSkL1nVWzU




Kindly subscribe to see more videos on this subject.

[Click here to SUBSCRIBE](#)

Subject: Network Theory (Network Analysis) (17EC35)


Other some important Question paper problems

Click on corresponding You-tube video link to for the solution.

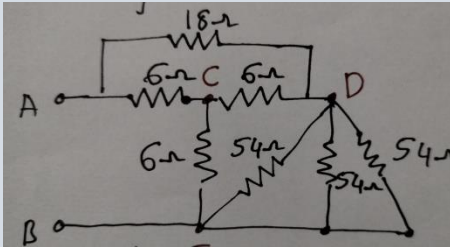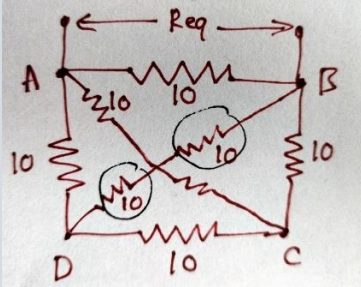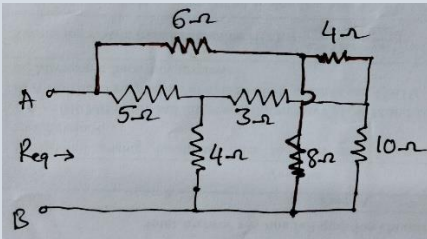1	<p>Find equivalent resistance between A and B using star delta transformation</p> 	https://youtu.be/SwWkqX6rOSw
2	<p>Find equivalent resistance between A and B using star delta transformation</p> 	https://youtu.be/P2kV2NOXbU0
3	<p>Find equivalent resistance between A and B using star delta transformation</p> 	https://youtu.be/AjKCY48Atlo

4

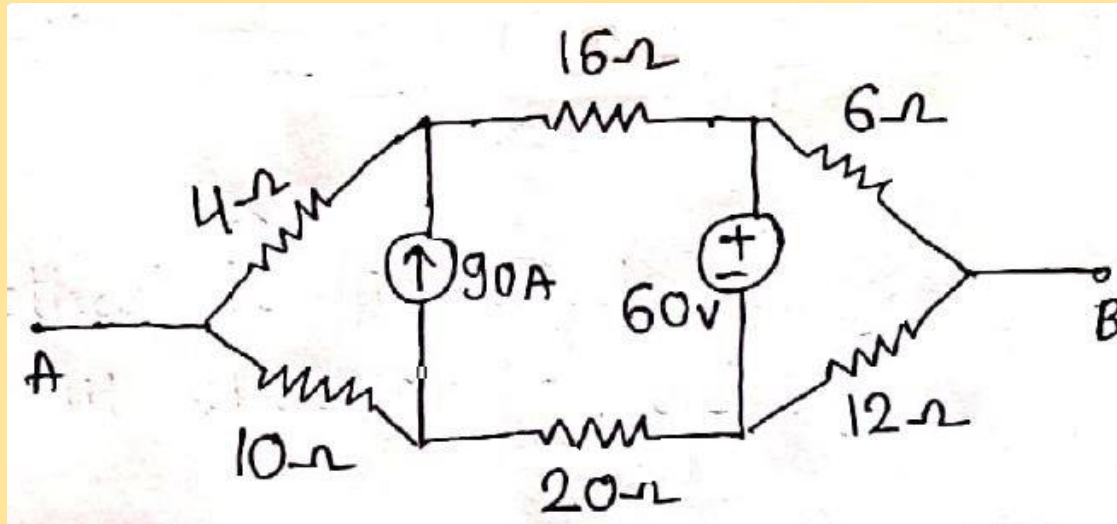
Reduce the Network shown below to a single voltage source in series with a resistance using source shift and source transformation.



<https://youtu.be/DBsQHdxYpi8>

5

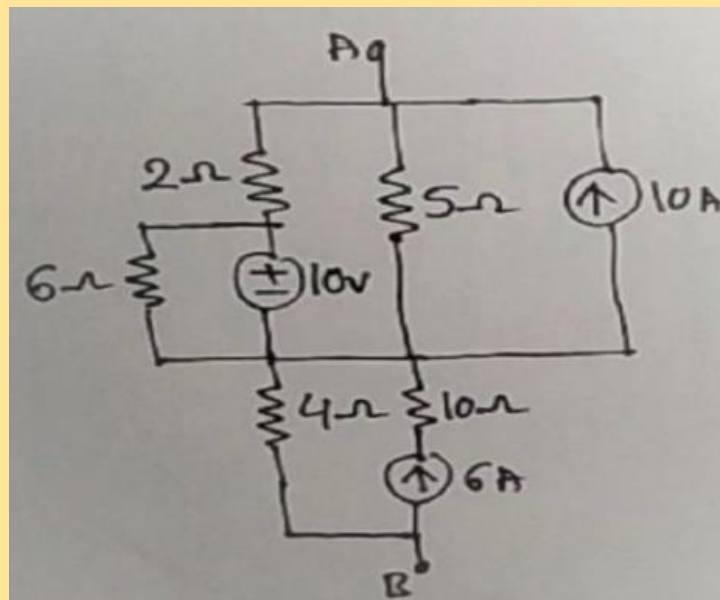
Find equivalent resistance between terminal A and B, using source transformation and shifting.



<https://youtu.be/9QUej3-ql1o>

6

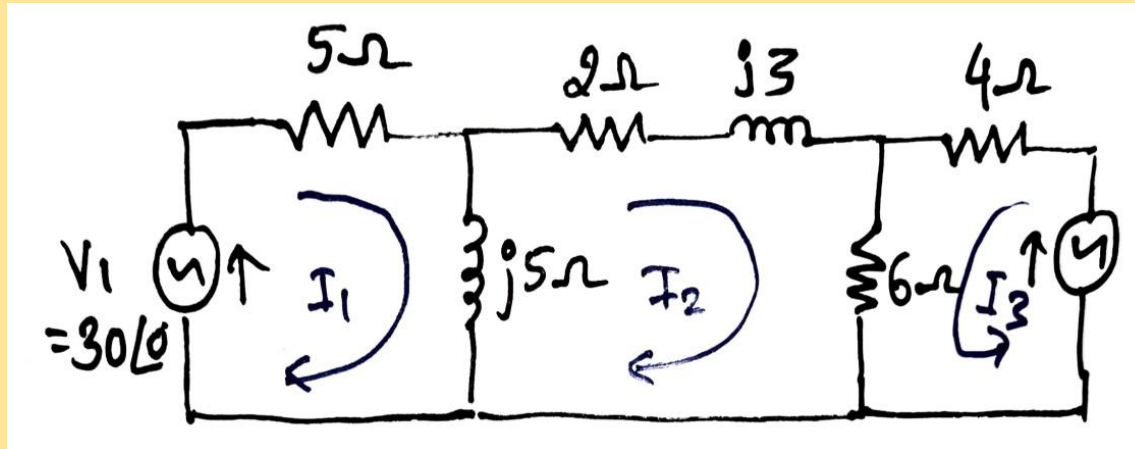In the Network shown below, Find voltage V_2 such that the current in the impedance $(2+j3) \Omega$ is zero. Use Mesh analysis.




<https://youtu.be/BqVW0BDvuY0>

7

For the circuit shown below, has zero capacitor voltage and zero inductor current when the switch k is open. At $t=0$, the switch k is closed. Solve for

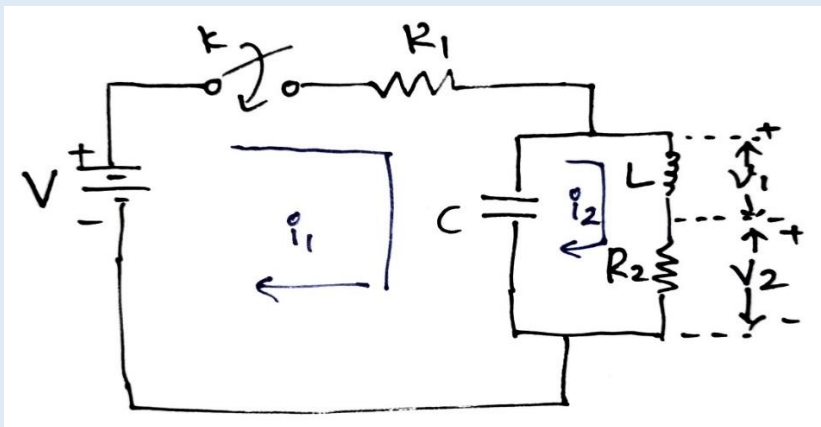
- i) V_1 and V_2 at $t = 0^+$
- ii) $\frac{dv_1}{dt}$, $\frac{d^2v_2}{dt^2}$ at $t = 0^+$
- iii) $\frac{dv_1}{dt}$, $\frac{d^2v_2}{dt^2}$ at $t = \infty$



<https://youtu.be/m11iom05SXc>

8

Determine ABCD or Transmission or General parameters
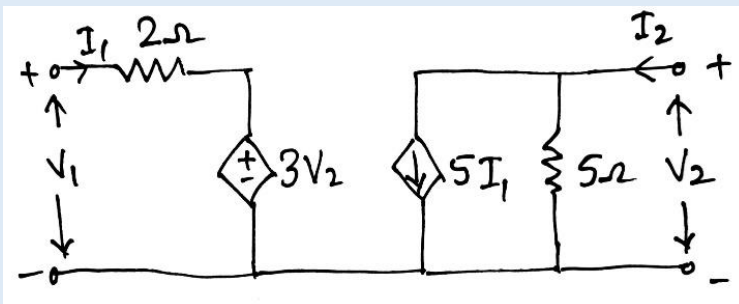
<https://youtu.be/MxKvOIMOTGA>

Kindly click on subscribe to see more videos on this subject.



[Click here to SUBSCRIBE](#)




Channel Name: Engg-Course-Made-Easy **SUBSCRIBE**




Subject: Electric Circuit Analysis (18EE32)
(Network Theory) (Network Analysis)




Solution for Jan.2021 Question paper




Click on corresponding You-tube video link to for the solution.

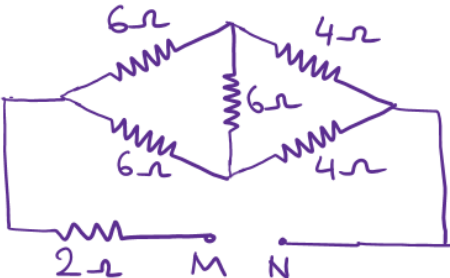
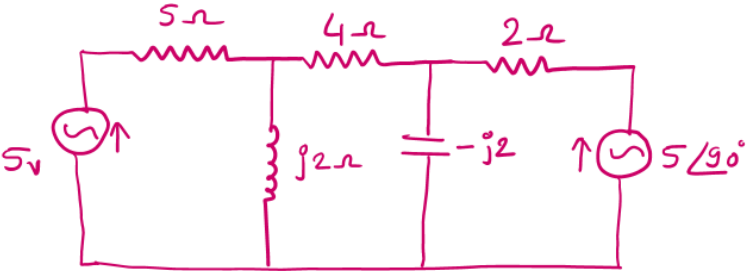
1 b.	<p>For the circuit shown below, determine resistance between M and N using star delta transformation.</p> 	https://youtu.be/D1LwIpQuoN8
1 c.	<p>Use node voltage analysis to find node voltages</p> 	https://youtu.be/mdFpYyo4g3c
2 a.	<p>Derive an expression for converting delta to star</p>	https://youtu.be/e-dh529iJAU

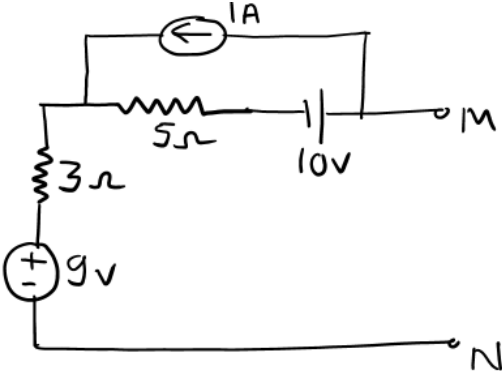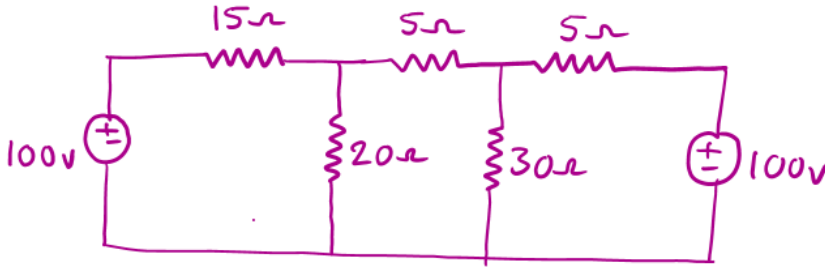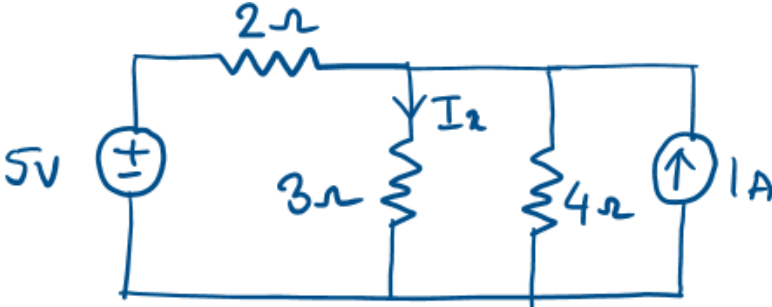2 b.	<p>Determine potential difference between M and N using source transformation.</p> 	<p>https://youtu.be/ck4RO0EVXGo</p>
2 c.	<p>Use mesh current analysis to find current through 30Ω.</p> 	<p>https://youtu.be/ROKacbmPbB8</p>
3 a.	<p>State and prove reciprocity theorem.</p>	<p>https://youtu.be/QzD6GLs1yQw</p>
3b.	<p>Find I_x using superposition theorem.</p> 	<p>https://youtu.be/GVWmGnkB-5w</p>

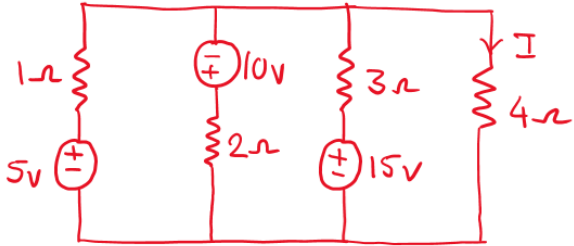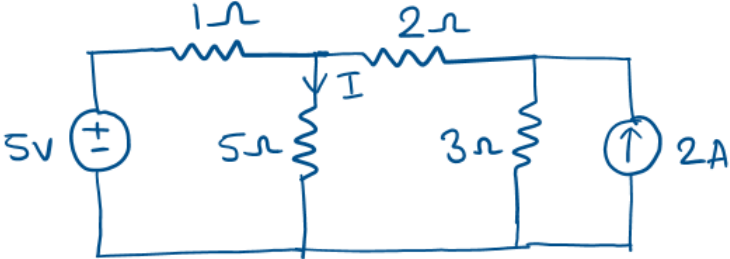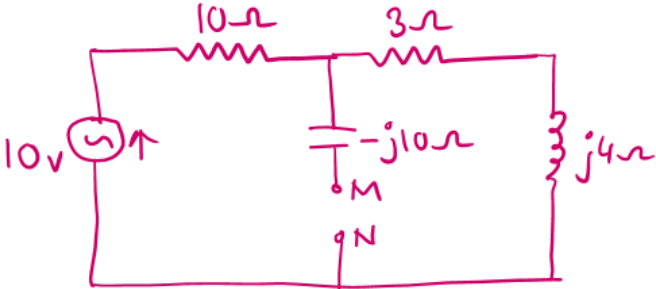3 c.	<p>Use Millman's theorem to find current I in the circuit.</p> 	https://youtu.be/xVdPFveri8w
4 a.	<p>State and obtain condition for maximum power when load impedance is equal to pure variable resistance.</p>	https://youtu.be/i8269fBfNXY
4 b.	<p>Find current I using Norton's theorem.</p> 	https://youtu.be/0DxtAa0fBw4
4 c.	<p>For the network shown below, draw Thevenin's equivalent circuit.</p> 	https://youtu.be/H0-sTqe02XA
5 a.	<p>Show that resonant frequency is the geometric mean of two half power frequencies.</p>	https://youtu.be/E6Gd9JDngnw
5 b.	<p>A series RLC circuit has a resistance of 10Ω, L= 0.5 H and C=0.4μF. Find i) resonant frequency, half power frequencies, bandwidth and quality factor.</p>	https://youtu.be/cRDq8OLscho

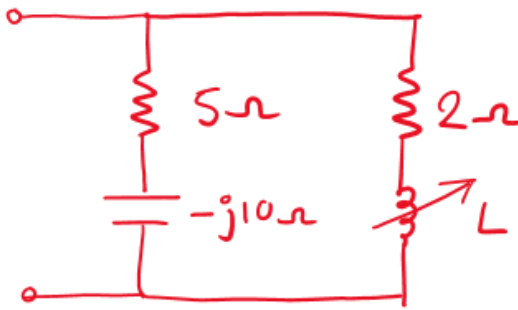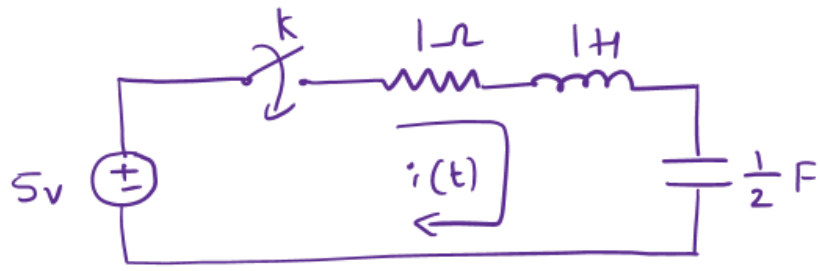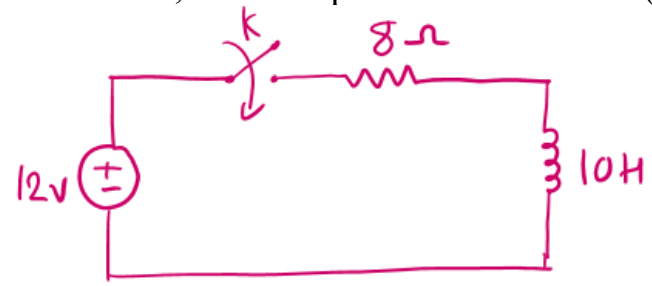5 c.	<p>For the network shown below, find the value of inductance take $\omega=500\text{r/s}$.</p> 	https://youtu.be/Ci24Yfx_kVA
6 a.	<p>Explain the behavior of R, L and C for initial condition.</p>	
6 b.	<p>For the network shown below, switch is closed at $t=0$. Determine the current and its first and second derivative at $t = 0^+$</p> 	https://youtu.be/nhQRoCYtRnI
6 c.	<p>For R-L circuit shown below, obtain expression for current $i(t)$ for $t \geq 0$.</p> 	https://youtu.be/j7osfKpiTT4
7 a.	<p>State and prove initial value theorem.</p>	https://youtu.be/6CYsSUIcvNk
7 b.	<p>Find inverse Laplace transform of $V(s) = \frac{10}{s(s+1)(s+2)}$</p>	https://youtu.be/83yJBE4B84E

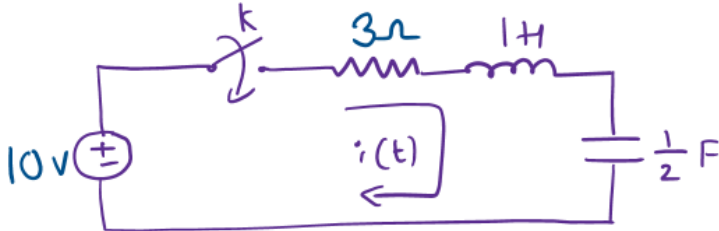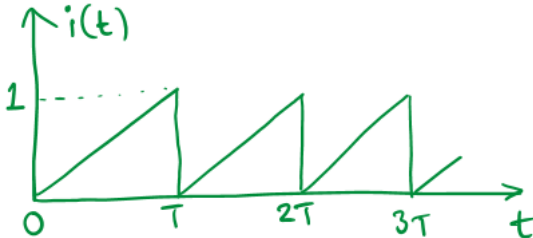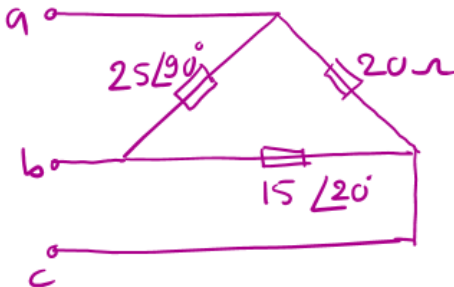7 c.	<p>For the network shown below, draw the transformed circuit and obtain the expression for current $i(t)$ for $t \geq 0$.</p> 	https://youtu.be/OCGLbowbynQ
8 a.	<p>Find LT of: i) Step signal ii) Ramp iii) Impulse signal</p>	https://youtu.be/IfEx_2U28gw
8 b.	<p>For the waveform shown below, obtain the Laplace transform.</p> 	https://youtu.be/gfbpMR78Wcs
8 c.	<p>Find the initial and final values of following functions: i) $V_1(s) = \frac{s^2+3s+2}{s^3+3s^2+3s+1}$ ii) $V_1(s) = \frac{10}{s(s+3)}$</p>	https://youtu.be/mNzfBgMYEa0
9 a.	<p>A 3-phase supply with line voltage of 250V has a unbalanced Delta connected load as shown in Fig. Determine line currents, active and reactive power for phase sequence ABC</p> 	

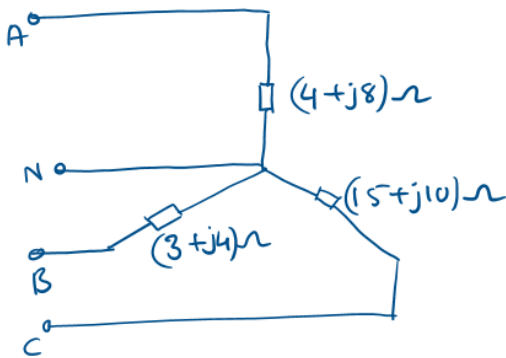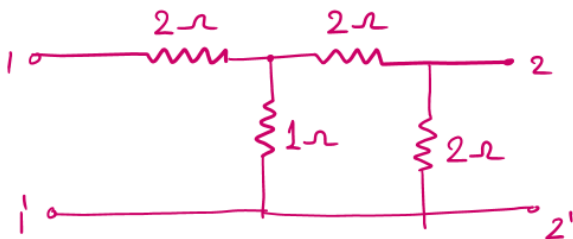9 b.	<p>An unbalanced 4 wire star connected load has a balanced supply of 400V. For the phase sequence ABC, calculate the line currents and total power of the circuit shown in figure.</p> 	
10a	Obtain the impedance parameters in terms of Admittance parameters.	https://youtu.be/ro55flsznd8
10b	<p>For the network shown below, determine z-parameters.</p> 	https://youtu.be/FG2hG06Vj_I

Kindly subscribe to see more videos on this subject.



SUBSCRIBE

Channel Name: Engg-Course-Made-Easy [SUBSCRIBE](#)

Subject: Electric Circuit Analysis (18EE32)
(Network Theory) (Network Analysis)


Solution for Sept.2020 Question paper

Click on corresponding You-tube video link to for the solution.

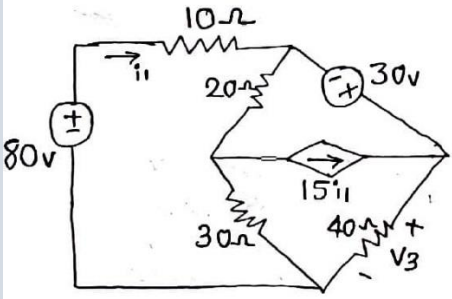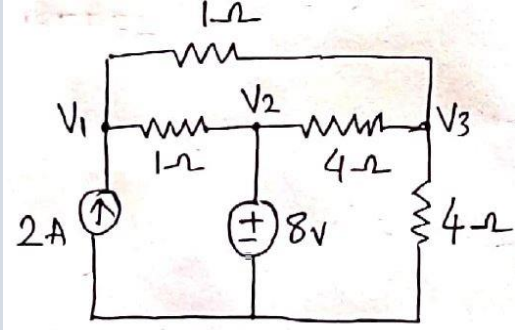
1a.	<p>Determine Voltage V_3 using mesh analysis.</p> 	<p><u>https://youtu.be/eCt1o_qRYDs</u></p>
1b.	<p>Find V_1, V_2, V_3 using node analysis.</p> 	<p><u>https://youtu.be/QcJowGkCJ5M</u></p>

1c.


Find equivalent resistance between A and B.

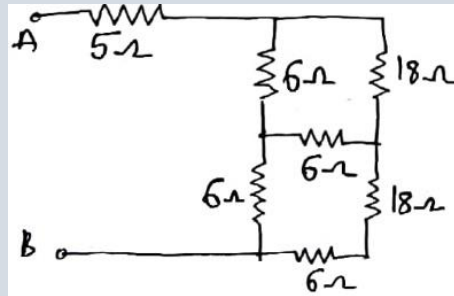
<https://youtu.be/C6CDc0rKOKA>

2a.

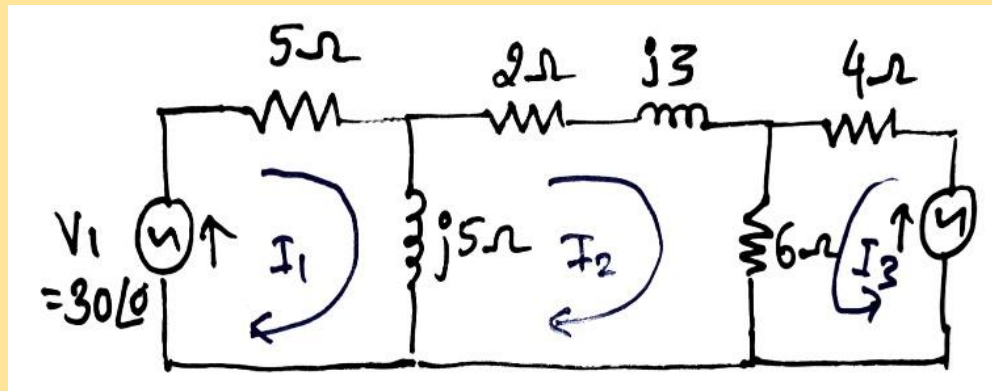
Find V using loop analysis.
<https://youtu.be/PRYPVxA0plw>

2b.

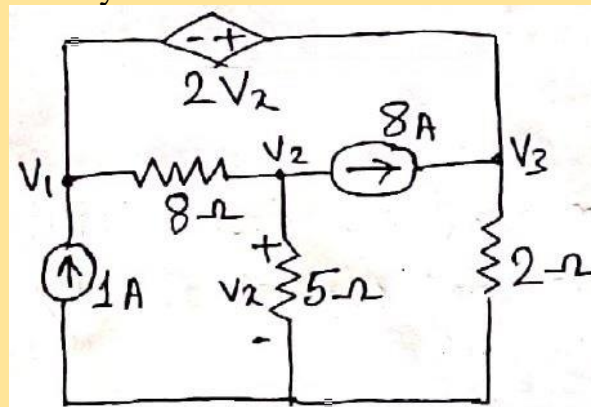Find V_x using Node analysis.
<https://youtu.be/hP45GKwFo-Q>

2c.

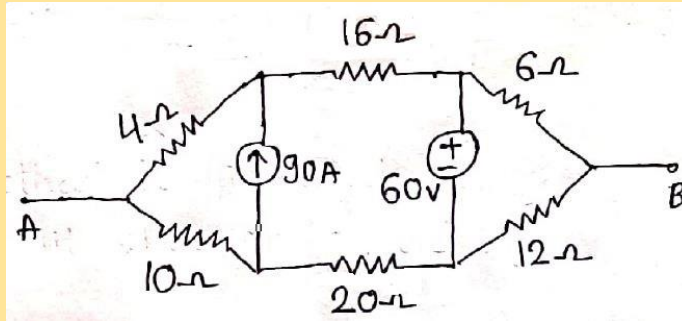
Reduce the network using source transformation and shifting.



<https://youtu.be/DBsQHdxYpi8>

3a.

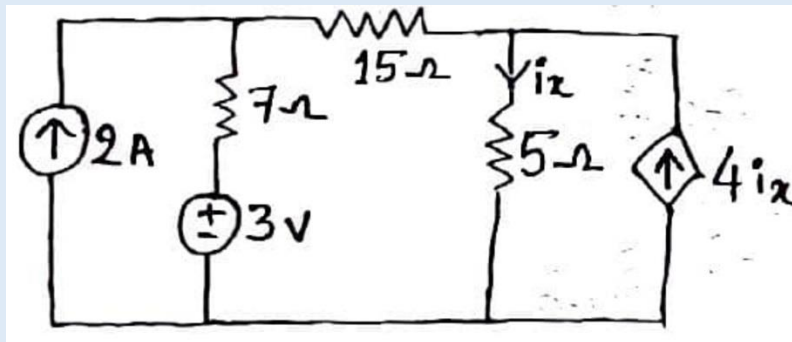
Find current i_x using superposition theorem.





https://youtu.be/dem_91MjoE4



3b.



Determine Thevenin's equivalent circuit.


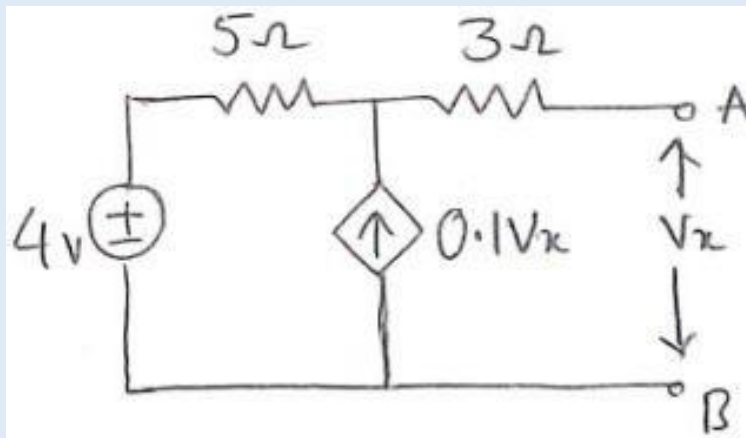




<https://youtu.be/pTD8ug3Zqy8>

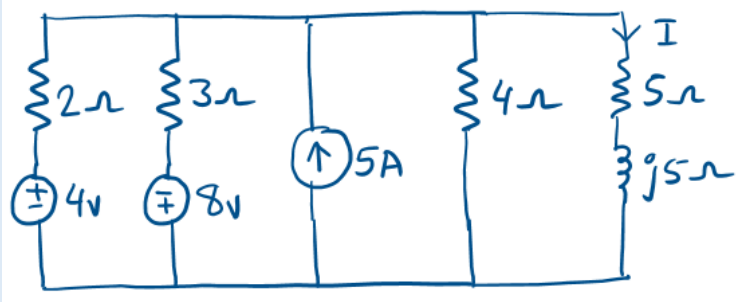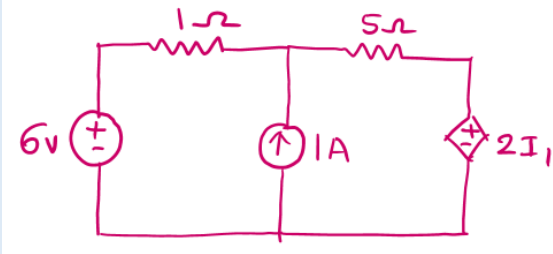3c.	<p>Use Millman's theorem to find current I, for the circuit shown below.</p> 	<p>https://youtu.be/zmR0OTTg9fU</p>
4a.	<p>Determine current through $1\ \Omega$ resistor using Norton's theorem, for the circuit shown below</p> 	<p>https://youtu.be/M5zxLnwiCwQ</p>
4b.	<p>Determine load resistor R_L to receive maximum power from the source. Also find the maximum power delivered to the load in the circuit shown below.</p>	
4c.	<p>State and verify reciprocity theorem for the circuit shown below.</p>	<p>https://youtu.be/QzD6GLs1yQw (Statement)</p>

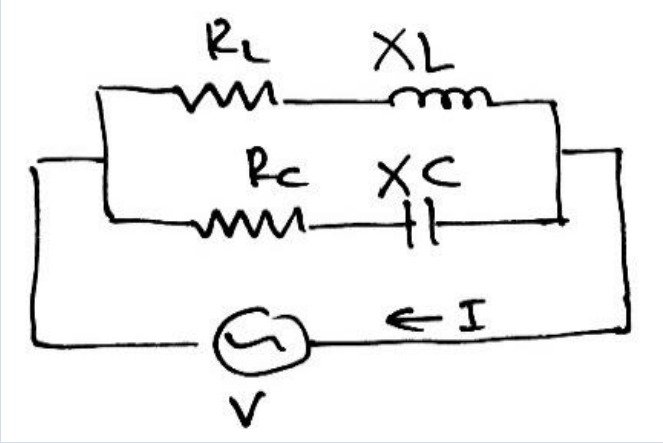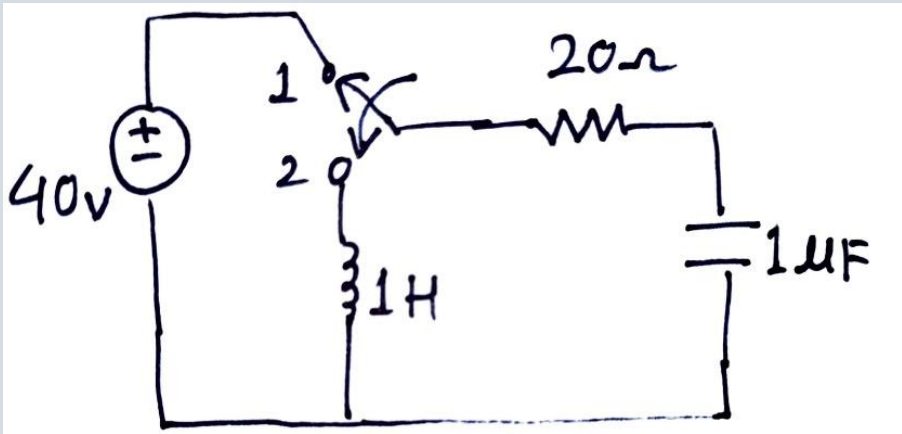5a.	<p>Derive the expression for resonant frequency.</p> 	<p>https://youtu.be/mY9Zvi2x2mk</p>
5b.	<p>An impedance coil having a resistance of 4Ω and an inductance of 1mH connected in series with $10\mu\text{F}$ capacitor.</p> <p>Determine Resonant frequency, Half power frequencies, impedance at resonance, Q of the circuit and Bandwidth.</p>	<p>https://youtu.be/kocfkaGg8w0</p>
5c.	<p>In the network shown below, the switch k is changed position from a to b at $t = 0$, the steady state is reached at position a.</p> <p>Find i, $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.</p> 	<p>https://youtu.be/s_dSHq1xdPE</p>

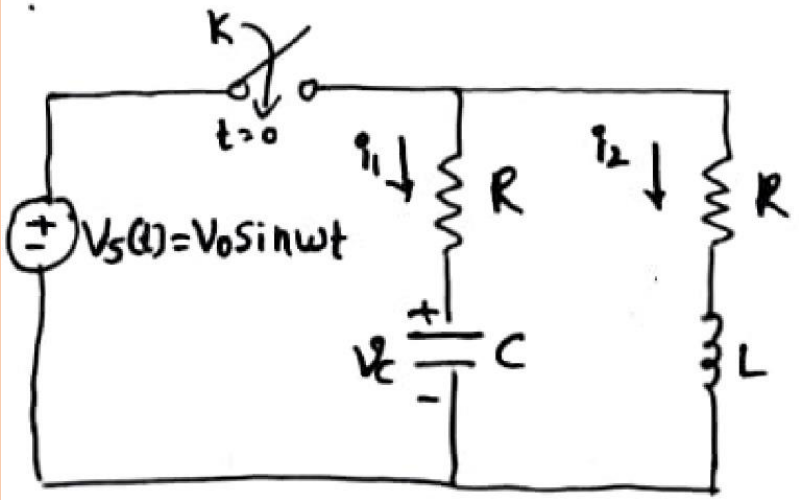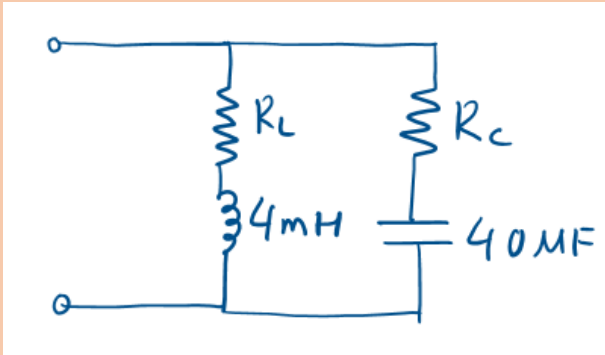6a.	<p>Find $\frac{di_1}{dt}$, $\frac{di_2}{dt}$ at $t = 0^+$.</p> 	https://youtu.be/aj785r6ULJ8
6b.	<p>Determine RL and RC for which the circuit shown in figure resonates at all frequencies</p> 	https://youtu.be/1jIAX3Rp6hI
6c.	<p>Show that resonant frequency of series resonant circuit is equal to the geometric mean of two half power frequencies.</p>	https://youtu.be/E6Gd9JDngnw
7a.	<p>State and prove initial and final value theorem in Laplace transformation</p>	https://youtu.be/6CYsSUIcvNk

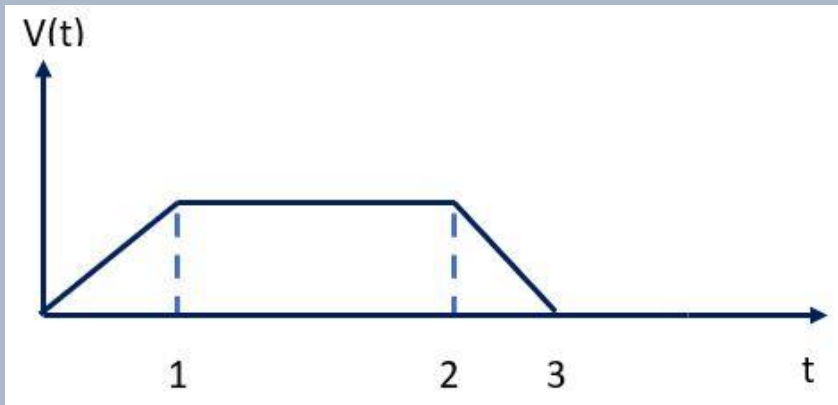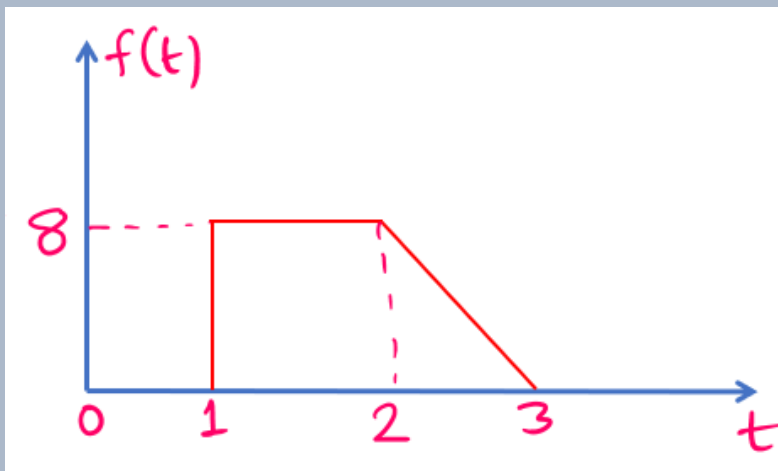7b.	Find Laplace transform of the given waveform. 	https://youtu.be/wgt0WnLFiol
7c.	Find Laplace transform of unit step function	https://youtu.be/IfEx_2U28gw
8a.	State and prove shifting theorem	https://youtu.be/9z4zZUuTtSU
8b.	Verify initial value theorem, given $f(t) = 10e^{5t}$	
8c.	Find Laplace transform of the signal shown below 	https://youtu.be/fRJmY8UxOsA
9a.	Three impedances $Z_1 = 20\angle 30^\circ \Omega$, $Z_2 = 40\angle 60^\circ \Omega$ and $Z_3 = 10\angle -90^\circ \Omega$ are delta connected to a 400V, 3-phase system as shown below. Determine the i) Phase currents and ii) Line currents	

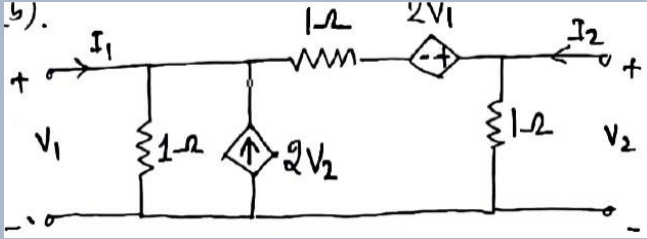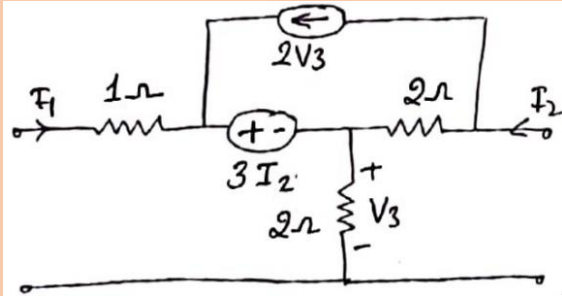9b.	<p>Find Y parameters.</p> 	https://youtu.be/LHxxZA-0HtI
9c.	<p>Express Y parameters in terms of Z parameters.</p>	https://youtu.be/LTxQBrd4EHo
10a.	<p>A unbalanced four wire star connected load has a balanced voltage of 400V, the loads are $Z_1=(4+j8) \Omega$, $Z_2=(3+j4) \Omega$, $Z_3=(15+j20) \Omega$. Calculate i) Line currents ii) Current in the neutral wire</p>	
10b.	<p>Find Z and T parameters.</p> 	https://youtu.be/HjGAFepsHeU
10c.	<p>Define H parameters with necessary equations</p>	

Kindly subscribe to see more videos on this subject.



SUBSCRIBE

Channel Name: **Engg-Course-Made-Easy** [SUBSCRIBE](#)


Subject: Electric Circuit Analysis (18EE32)
(Network Theory) (Network Analysis)

Solution for Dec-2019/Jan.2020 Question paper

Click on corresponding You-tube video link to for the solution.

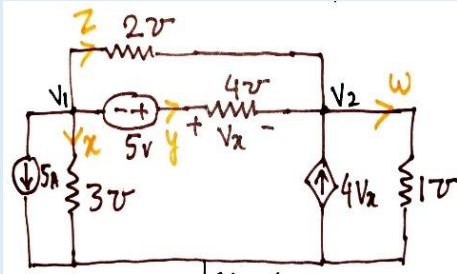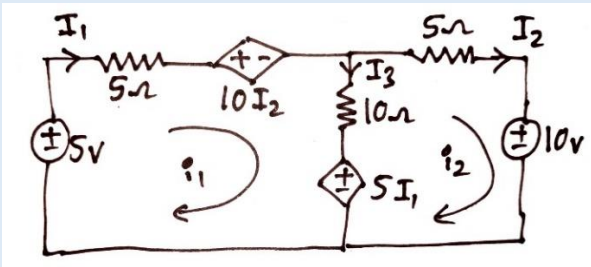
	Problem	You-Tube Link for solution
1 a)	<p>Setup nodal equations for the circuit of Fig. Q1(a) and then find the power supplied by 5 – V source.</p> 	https://youtu.be/pqOEakh5o0M
1 b)	<p>Making use of source shifting procedure, simplify the circuit of Fig. Q1(b) in such a way that the voltage Vx is determined.</p>	
1 c)	<p>Use mesh analysis to determine the branch currents in the network indicated in Fig. Q1(c).</p> 	https://youtu.be/t-P9oRppOv0

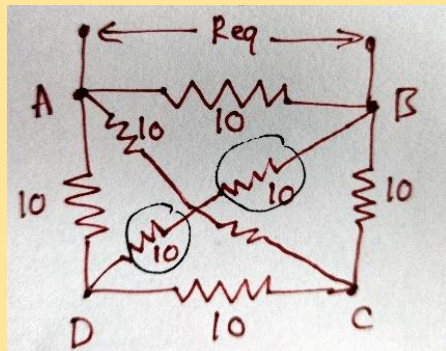Find Req' for the network shown in Fig. Q2(a) across A and B.




<https://youtu.be/P2kV2NOXbU0>

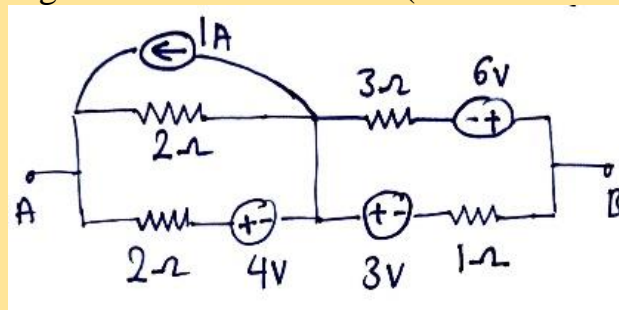Reduce the network of Fig. 22(c) to a form with only one current source across terminals using source transformation (terminals A and B).






<https://youtu.be/Mg7lfr9VjnM>

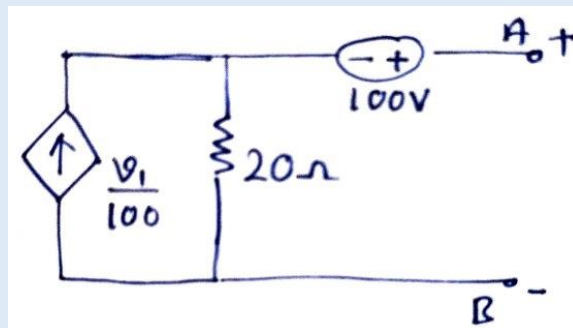
Find the Thevenin's equivalent circuit at the terminals A and B of the circuit in Fig. Q3(a).



<https://youtu.be/95toHh8Izxc>

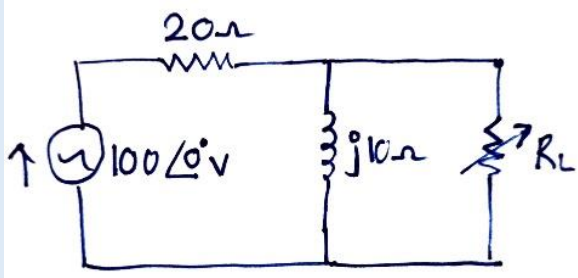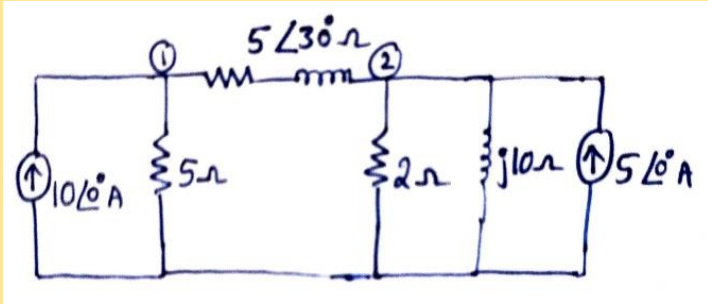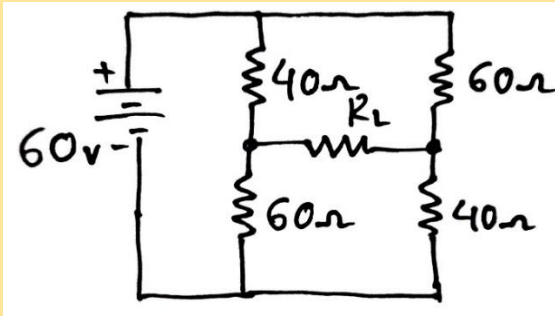3 b)	<p>Find the value of R_L in the network shown in Fig. Q3(b) that will absorb a maximum power and specify the value of that power.</p> 	https://youtu.be/XSjhU_yMvkg
3c)	<p>In the network shown in Fig. Q3(c) the voltage source of 5V causes a current I in the 20Ω resistor. Find I. Verify the reciprocity theorem.</p>	
4 a)	<p>In the network shown in Fig. Q4(a) determine the nodal voltage V, using superposition theorem.</p> 	https://youtu.be/VrdsfYKI_yc
4 b)	<p>Use Thevenin's theorem to find current in $R_L = 62$ in Fig. Q4(b).</p> 	https://youtu.be/VBp2jKNAQ7M
4 c)	<p>State and prove Millman's theorem.</p>	https://youtu.be/_a5HT5WRCMY

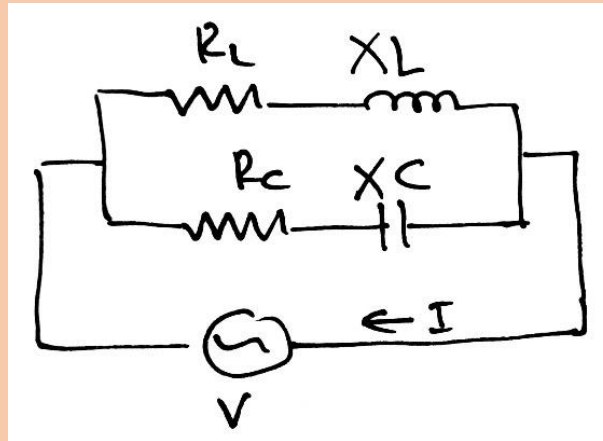
Derive the expression for resonant frequency for the general parallel resonant circuit shown below.




<https://youtu.be/mY9Zvi2x2mk>


For the circuit shown below, has zero capacitor voltage and zero inductor current when the switch k is open. At $t=0$, the switch k is closed. Solve for

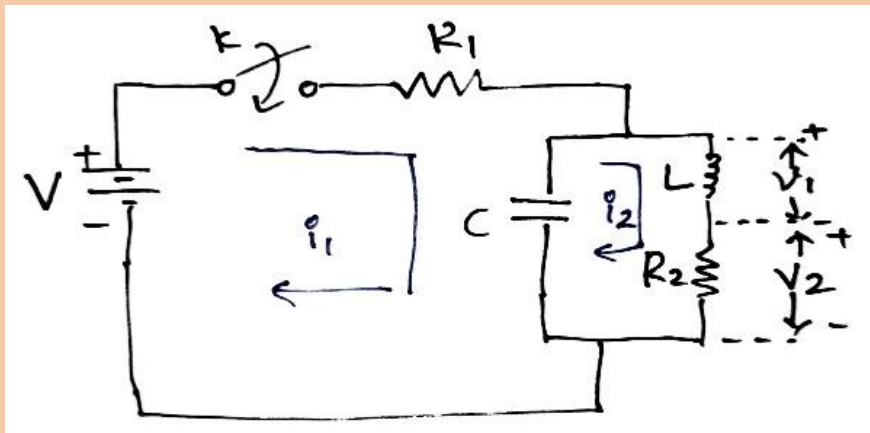- i) V_1 and V_2 at $t = 0^+$
- ii) $\frac{dv_1}{dt}$, $\frac{d^2v_2}{dt^2}$ at $t = 0^+$
- iii) $\frac{dv_1}{dt}$, $\frac{d^2v_2}{dt^2}$ at $t = \infty$



<https://youtu.be/m11iom05SXc>

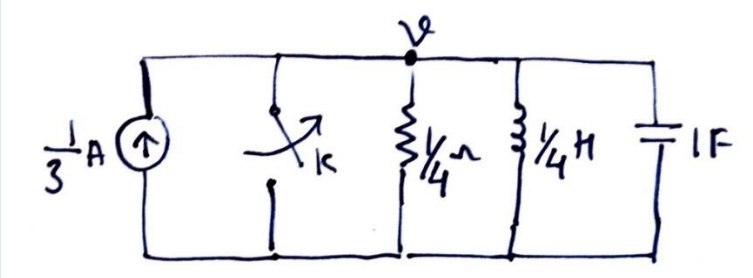6 a)	<p>Circuit shows RLC parallel circuit excited by a DC current source. At $t=0$, the switch k is opened. Find $V(t)$.</p> 	https://youtu.be/-cXYdCY5u6Q
6 b)	<p>A 400Hz AC source is connected in series with a capacitor and a coil whose resistance and inductance are $20\text{m}\Omega$ and 6mH respectively. If the circuit is in resonance at 200Hz, Find i) Value of Capacitor ii) Voltage across capacitor. iii) Maximum energy stored. iv) Half power frequencies</p>	https://youtu.be/sNfnpgC_GR4
6c)	<p>What are initial conditions in network? Write the equivalent form of the network elements in terms of the initial conditions</p>	
7a)	<p>Find Laplace transform of the square wave shown below.</p>	https://youtu.be/OcjdYov6204 (replace 'T' by 'a' in video)
7b)	<p>Fig. shows a series RLC circuit excited by a voltage $V(t)=12 \sin 5t$. The initial current in the circuit is 5A and the initial voltage across capacitor is 1V with polarity shown. Find $i(t)$ using Laplace transformation method.</p>	
7c)	<p>State and prove initial value theorem in the context of Laplace transformation</p>	https://youtu.be/6CYsSUIcvNk
8a)	<p>A rectangular voltage pulse of unit height and duration 'T' is applied to a series R-C combination at $t=0$. Determine voltage across capacitance 'C' as a function of time. Use Laplace Transformation method.</p>	https://youtu.be/PgNK_MrEbPQ
8b)	<p>Find the Laplace Transforms of the two different functions given below and sketch the waveforms.</p>	
9a)	<p>A symmetrical 3-ϕ, 100 V, 3-wire supply feeds an unbalanced star connected load with impedance of the load as $Z_R = 5\angle 0^\circ \Omega$, $Z_Y = 2\angle 90^\circ \Omega$ and $Z_B = 4\angle -90^\circ \Omega$. Find the line currents, voltage across impedances and displacement natural voltage. Also calculate the power consumed by the load. Draw phasor diagram sequence RYB. Take VR_Y as reference.</p>	

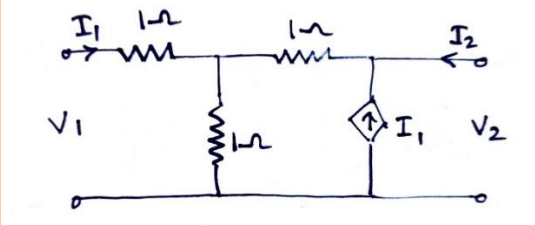9 b)	<p>Find Z and ABCD parameters. Find whether the network is Reciprocal? Or Symmetrical?</p> 	https://youtu.be/iSx1Q7MAQpk
10a)	<p>A 3-ϕ delta connected load has $Z_{RY} = (100 + j50)\Omega$, $Z_{YB} = (20 - j75)\Omega$ and $Z_{BR} = (70.7 + j70.7)\Omega$ and it is connected to balanced 3-ϕ, 400V supply. Determine the line currents, power consumed by the load. Sketch the phasor diagrams. Assume RYB phase sequence and take V_{YB} as the reference phasor.</p>	
10b)	<p>For the circuit shown below, find Y parameters. Is the network symmetrical? Or Reciprocal?</p>	

Kindly subscribe to see more videos on this subject.

[Click here to SUBSCRIBE](#)